

Saathi

Date 28/2/19

MOS DEVICE characteristics

- $I_{D,sat} = \mu C_{ox} \left(\frac{W}{L} \right) \frac{(V_{GS} - V_{th})^2}{2} (1 + \lambda V_{DS})$

$I_{D,sat} \propto \left(\frac{W}{L} \right)$ linear relationship

$I_{D,act} \propto (V_{GS} - V_{th})^2$ parabolic relationship


$I_{D,sat} \propto (1 + \lambda V_{DS})$ small signal linearity

- Load line equation :- $V_{DS} = V_{DD} - I_D R_D$

- Pinch off voltage :- boundary betⁿ triode region and saturation region

$V_p = V_{GS} - V_{th}$

- slope of load line = $-1/R_D$

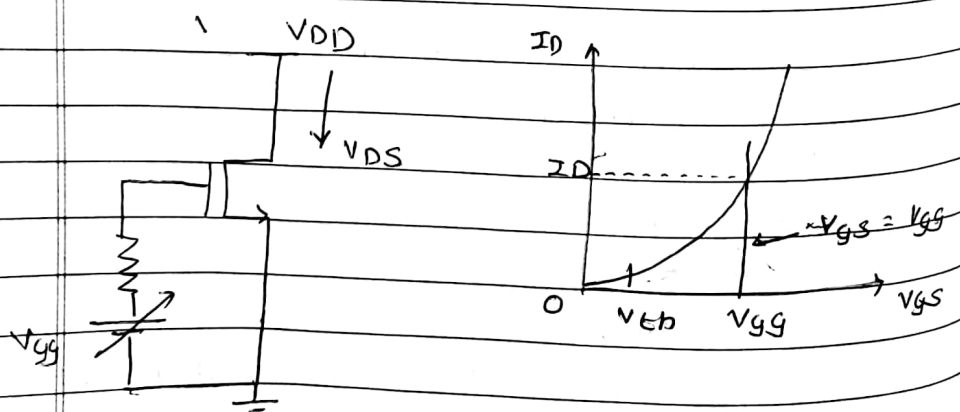

Loop equation, $V_{GS} = V_{GG}$

athi

Date ___/___/___

Saathi

1) Given an operational amp with $R_i = \infty$, $A = 10^4$, $R_o = 0 \Omega$. Find V_o , if $V_p = 750.25 \text{ mV}$, $V_n = 751.75 \text{ mV}$

$$\begin{aligned} V_o &= A(V_p - V_n) \\ &= 10^4(750.25 - 751.75) \times 10^{-3} \\ &= -15 \text{ V.} \end{aligned}$$

2) Find V_n if $V_o = -5 \text{ V}$, $V_p = 0$. (op-amp is same)

$$\begin{aligned} V_o &= -A V_n \\ V_n &= \frac{-5}{-10^4} \\ V_n &= 5 \times 10^{-4} \text{ V.} \end{aligned}$$

3) Find V_p , if $V_o = V_n = 5 \text{ V}$

$$\begin{aligned} V_o &= A(V_p - V_n) \\ V_o + A V_n &= V_p \\ A &= 10^4 \\ V_p &= 5.0005 \text{ V} \end{aligned}$$

4) Find V_n , if $-V_o = V_p = 1 \text{ V}$


$$\begin{aligned} -1 &= 10^5(1 - V_n) \\ V_n &= \frac{10^4 + 1}{10^4} \\ &= 1.0001 \end{aligned}$$

5) In the voltage amplifier circuit shown below, let $V_s = 100 \text{ mV}$, $R_s = 100 \text{ k}\Omega$, $V_i = 75 \text{ mV}$, $R_L = 10 \Omega$

Saathi

Date ___/___/___

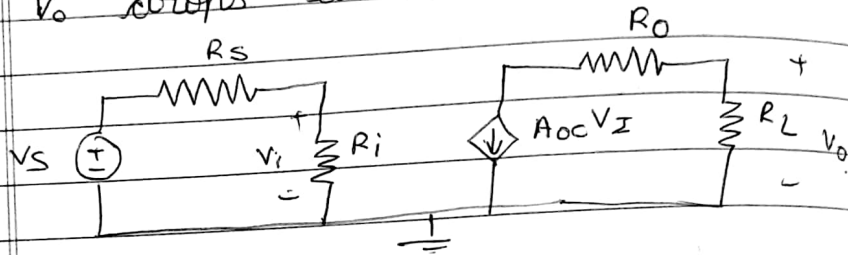$V_o = 2V$. If connecting a 30Ω resistance in parallel with R_L , V_o drops to $1.8V$. Find R_i , A_{oc} & R_o .



Sol: Given:- $V_s = 100mV$ $R_s = 100K\Omega$
 $V_i = 75mV$ $R_L = 10\Omega$

Given $I_s = \frac{250 \times 10^{-3}}{100 \times 10^3}$
 $= \frac{1}{4} \times 10^{-6}$
 $= 0.25 \times 10^{-6} A$

$R_i = \frac{75 \times 10^{-3}}{0.25 \times 10^{-6}}$
 $R_i = 300 K\Omega$

$V_o - I R_o + A_{oc} V_i \frac{R_L}{R_L} = 0$
 $V_o + A_{oc} V_i R_i = I R_o$
 $\frac{V_o}{R_L} = I$
 $\frac{2}{10} = I$
 $0.2 A = I$
 A_{oc}

Instead of A_F only A is given, it is feedback gain.

Date ___/___/___

Saathi

$$2 + A_{oc}(75 \times 10^{-3}) = 0.2 R_0$$

$$2 R_0 - A_{oc}(75 \times 10^{-3}) = -20 \quad \text{--- (1)}$$

case ii): - $R = 30 \parallel R_L$

$$R_{eff} = \frac{30 \times 10}{40} = 7.5 \Omega$$

$$V_0 = \frac{A_{oc} V_{in}}{R_0 + 7.5}$$

$$1.8 = \frac{A_{oc}(75 \times 10^{-3})(7.5)}{R_0 + 7.5}$$


$$1.8 R_0 + 13.5 = 562.5 A_{oc} \times 10^{-3}$$

$$1.8 R_0 - 562.5 \times 10^{-3} A_{oc} = -13.5 \quad \text{--- (2)}$$

$$R_0 = 5 \Omega$$

$$A_{oc} = 40$$

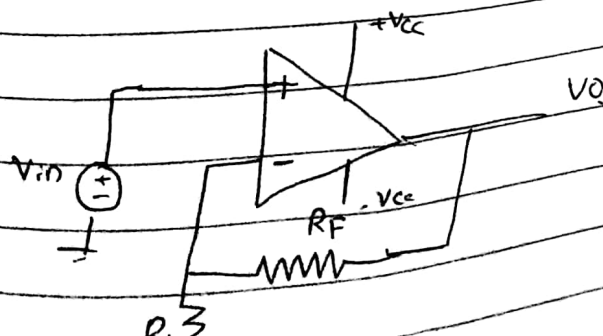e) Design a non-inverting amplifier whose gain is variable over the range $1V/V \leq A_F \leq 5V/V$, by the means of $100 K\Omega$ potentiometer. Repeat the above problem for a gain $0.5V/V \leq A_F \leq 2V/V$.



Practical devices will have Voltage divider circuit.

(Saathi)

Date ___/___/___

Sol: i) For minimum gain value = 1

$$A_F = 1 + \frac{R_F}{R_1}$$

$$R_F = 0$$

$$A_F = 1$$


(potentiometer should be connected across R_F)

For maximum gain value = 5

$$R_F = 100 \text{ k}\Omega \quad (\text{it should be maximum})$$

$$5 = 1 + \frac{100 \times 10^3}{R_1}$$

$$R_1 = 25 \text{ k}\Omega$$

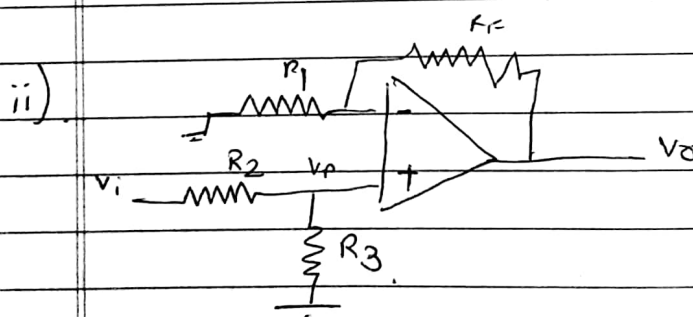

$$V_p = \frac{V_i \times R_3}{R_2 + R_3}$$

$$V_o = \left(1 + \frac{R_F}{R_1} \right) V_p$$

$$= \left(1 + \frac{R_F}{R_1} \right) \left(\frac{R_3}{R_2 + R_3} \right) V_i$$

$$\text{If } R_F = 0$$

$$R_2 = R_3$$

$$= (1) \left(\frac{1}{2} \right) V_i$$

ltage

Saathi

= 1

meter should
be connected across

= 5

should be
(sum)

Date ___/___/___

Saathi

$$V_o = 0.5 V$$

V_i

$$\begin{cases} R_F = 0 \Omega \\ R_2 = R_3 \end{cases}$$

Maximum value:-

$$R_F = 100 K\Omega$$

$$A = 1 + \frac{R_F}{R_i}$$


$$2 = \left(1 + \left(\frac{100 \times 10^3}{R_i}\right)\right) \left(\frac{R_F}{2 R_3}\right)$$

$$R_F = 100 K\Omega$$

$$R_i = 33.3 K\Omega$$

$R_i =$

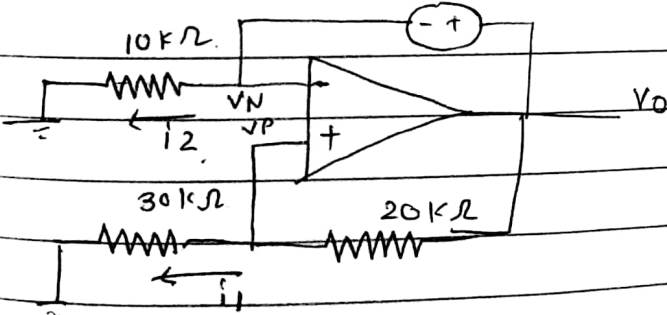7) Find V_N , V_P and V_o as well as power released by 4V source.



$$V_P = (30 \times 10^3) I_1$$

Because of virtual same voltage at inputs,

$$V_N = V_P$$

Voltage drop betⁿ

$$V_N \& V_o = V_P \& V_o$$

Saathi

Date ____ / ____ / ____

$$4 = I_1 \times 20 \times 10^3$$

$$\frac{4}{5 \times 10^3} = I_1$$

$$I_1 = 0.2 \times 10^{-3} \text{ A}$$

$$V_P = 6 \text{ V}$$

$$V_N = 6 \text{ V}$$

$$V_O - V_N = 4 \text{ V}$$

$$V_O = 10 \text{ V}$$

$$V_N = I_2 (10 \times 10^3)$$

$$\frac{6}{10^4} = I_2$$

$$6 \times 10^{-4} = I_2$$

$$P_{4V} = (4)(6 \times 10^{-4})$$
$$= 24 \times 10^{-4} \text{ W}$$


Sol:-

Saathi

Date ___/___/___

Saathi

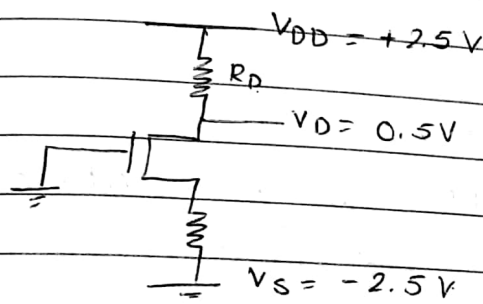1) Design a circuit shown below, such that the transistor operates at $I_D = 0.4 \text{ mA}$, $V_D = 0.5 \text{ V}$. NMOS transistor has $V_t = 0.7 \text{ V}$, $\mu_n C_{ox} = 100 \mu\text{A/V}^2$, $W/L = 32$, neglect λ .



sol - $I_D = 0.4 \text{ mA}$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2.5 - 0.5}{0.4 \times 10^{-3}} = 5 \text{ k}\Omega$$

MOS to be saturation $V_t > V_{GD}$
 $0.7 > -0.5$

MOSFET is in saturation

$$I_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$0.4 \times 10^{-3} = \frac{1}{2} \times 100 \times 10^{-6} (32) (V_{GS} - V_t)^2$$

$$1/2 = V_{GS} - 0.7$$

$$V_{GS} = 1.2 \text{ V}$$

$$V_S = -1.2 \text{ V}$$

$$R_S = \frac{-V_{SS} + V_S}{I_D}$$

$$= 3.25 \text{ k}\Omega$$

Saathi

Date ____/____/____

2) Redesign the circuit for the same circuit, $V_{DD} = -V_{SS} = 2.5V$, $V_t = 1V$, $\mu_p C_{ox} = 60 \mu A/V^2$, $(W/L) = 40$, $I_D = 0.3 mA$ and $V_D = 0.4V$.

Sol:- $I_D = 0.3 mA$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2.5 - 0.4}{0.3 \times 10^{-3}} = 7 k\Omega$$

$$V_t > V_{GD}$$

$$1 > -0.4$$

$\therefore$ MOSFET is in saturation region

$$I_D = \frac{1}{2} \mu_p \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$$

$$0.3 \times 10^{-3} = \frac{1}{2} \times 60 \times 10^{-6} \times 40 \times (V_{GS} - 1)^2$$

$$\frac{1}{4} = (V_{GS} - 1)^2$$

$$V_{GS} = 1.5V$$

$$V_{SS} = -1.5V$$

$$R_S = \frac{V_S - V_{SS}}{I_D}$$


$$= \frac{-1.5 + 2.5}{0.3}$$

$$R_S = 3.33 k\Omega$$

3) Design the circuit shown below, to obtain the current $I_D = 80 \mu A$ find the value required for R and V_D . (Given $V_t = 0.6V$, $\mu_p C_{ox} = 200 V^2$, $L = 0.8 \mu m$, $W = 4 \mu m$, $\lambda = 0$)

Date / /

Saathi

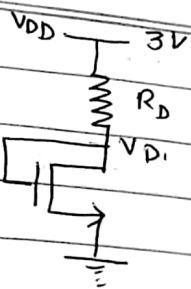

$$V_t = 0.6 \text{ V}$$

$$V_{DD} = 3 \text{ V}$$

$$V_G = V_D$$

$$V_{GD} = 0$$

$$\therefore V_t > V_{GD}$$

$\therefore$ MOSFET is in saturation region

$$I_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$80 \times 10^{-6} = \frac{1}{2} \times 200 \times 10^{-6} \left(\frac{4}{0.8} \right) (V_{GS} - 0.6)^2$$

$$0.4 + 0.6 = V_{GS}$$

$$V_{GS} = 1 \text{ V}$$

$$V_G = V_D = 1 \text{ V}$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{3 - 1}{80 \times 10^{-6}} = 25 \text{ k}\Omega$$

4) Redesign the circuit, to double the value of I_D , without changing V_D , give new values for (W/L) and R

$$V_D = 1 \text{ V}$$

$$I_D = 2 \times 80$$

$$= 160 \mu\text{A}$$

$$R_D = \frac{V_{DD} - V_D}{I_D}$$

$$= \frac{3 - 1}{160}$$

$$160$$

$$= 12.5 \text{ k}\Omega$$

Page No.

Saathi

Date ___ / ___ / ___

$$I_D = \frac{1}{2} k'_n \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

$$160 \times 10^{-6} = \frac{1}{2} \times 200 \times 10^{-6} \left(\frac{W}{L}\right) (1 - 0.6)^2$$

$$(W/L) = 10$$

$$W = 10 \times L$$


$$= 10 \times 0.8 \mu m$$

$$W = 8 \mu m$$

$$\frac{W}{L} = \frac{8 \mu m}{0.8 \mu m}$$

Sol:-

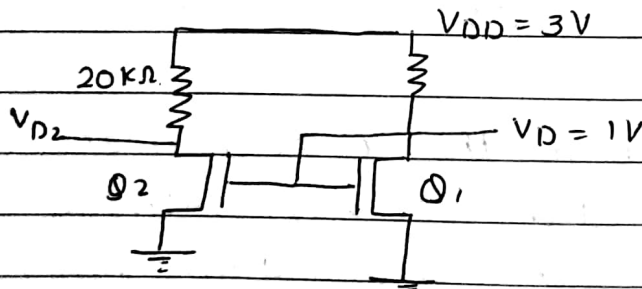5) Consider the circuit shown below, let the voltage V_D be applied to the gate of another transistor shown in fig. Assume Q_2 is identical to Q_1 . Find drain current and voltage of Q_2



Sol: $R = 25 k\Omega$

$$I_D = \frac{k'}{2} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

$$= \frac{1}{2} \times 200 \times 10^{-6} \left(\frac{4}{0.8}\right) (1 - 0.6)^2$$

$$I_D = 80 \mu A$$

$$V_{D2} = V_{DD} - I_D(20)$$

$$= 3 - (80 \times 10^{-6})(20 \times 10^3)$$

$$= 1.4 V$$


Page No.

Saathi

Date ___/___/___

Saathi

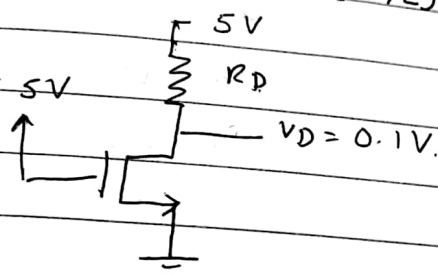Design the follⁿ circuit to establish drain voltage of 1V. What is the effective resistance betⁿ drain and source at this operating point (Given $V_t = 1V$, $k'_n (w/L) = 1mA/V^2$).



$$V_{GS} - V_t = 4V$$

$$V_{DS} = 0.1$$

$$V_{GS} - V_t > V_{DS}$$

MOSFET is in triode region

$$I_D = k'_n \left(\frac{w}{L} \right) \left((V_{GS} - V_t) V_{DS} - \frac{(V_{DS})^2}{2} \right)$$

$$= 10^{-3} \left((5-1)(0.1) - \frac{(0.1)^2}{2} \right)$$

$$= 3.95 \times 10^{-4} A$$

$$R_D = \frac{5 - 0.1}{3.95 \times 10^{-4}}$$

$$= 12,405 \text{ k}\Omega$$

$$r_{ds} = \frac{V_{DS}}{I_D} = \frac{0.1 \times 10^{-3}}{0.395}$$

$$= 253 \Omega$$

7) In the circuit in ex 6. if the value of R_D is doubled, find the approximate value of I_D & V_D .

Sol: R_D is doubled

$$V_D = \frac{0.1}{2}$$

$$= 0.05 \text{ V}$$


$$I_D = \frac{V_{DD} - V_D}{R_D}$$

$$= \frac{5 - 0.05}{24.8 \times 10^3}$$

$$= 0.199 \text{ mA}$$

$$\approx 0.2 \text{ mA}$$

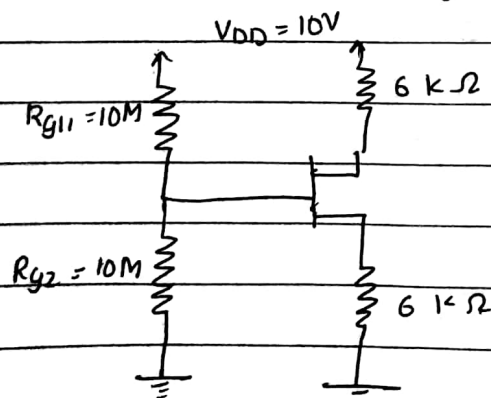8) Analyze the circuit shown below, determine the voltages at all nodes and current through all branches let $V_t = 1 \text{ V}$, $k'_n (W/L) = 1 \text{ mA/V}^2$. Neglect channel length modulation effect



Sol - $I_G = 0$

$$I_1 = I_2 = \frac{V_{DD}}{20\text{M}} = \frac{10}{20\text{M}} = 0.5 \times 10^{-6}$$

Date ___/___/___

Saathi

$$V_g = 5V$$

Assuming Q is in saturation

$$I_D = \frac{1}{2} K_n \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$V_D = 10 - I_D(6k)$$

$$V_S = I_S(6k)$$

$$V_{GS} = V_g - V_S$$

$$= 5 - I_S(6k)$$

$$I_D = (10^{-3})(5 - I_S(6k) - 1)^2$$

$$I_D = 10^{-3}(16 + 36I_D^2 k^2 - 48I_D k)$$

$$I_D = 0.5 \text{ mA}$$

$$\text{or } I_D = 0.88 \text{ mA}$$

$$V_S = 5.34 \text{ V}$$

$$V_{GS} = V_g - V_S = -0.34 \text{ V}$$

rejecting 0.88 mA

$$\therefore I_D = 0.5 \text{ mA}$$

$$V_S = 6 \times 0.5$$

$$= 3 \text{ V}$$

$$V_D = 10 - 6(0.5)$$

$$= 7 \text{ V}$$

$$V_{GS} = V_g - V_S$$

$$= 5 - 3 = 2$$

$$V_{GS} - V_t = 2 - 1 = 1$$

$$V_{DS} = 7 - 3 = 4 \text{ V}$$

$$V_{DS} > V_{GS} - V_t$$

assumption is correct

Saathi

Date ___/___/___

a) For the above circuit, what is largest value of R_D that can have while the transistor remains in the saturation mode

sol. At the edge of saturation

$$V_{DS} = V_{GS} - V_t$$

$$V_{DS(sat)} = 2 - 1 = 1V$$

The value of V_D to make $V_{DS} = 1V$

$$V_{DS} = V_D - V_S$$

$$V_D = 4$$

$$R_D(max) = \frac{V_{DD} - V_D}{I_D}$$

$$I_D$$

$$= \frac{10 - 4}{0.5mA}$$

$$0.5mA$$

$$= 12 k\Omega$$

10) Design the circuit shown below

so that MOSFET operates in

saturation region with $I_D = 0.5mA$,


$V_D = 3V$. Let the enhancement type

p-MOS have $V_t = -1V$, $k'_n(W/L) = 1mA/V^2$

$\lambda = 0$. What is the largest value

that R_D that can have while MOSFET

is in satⁿ region

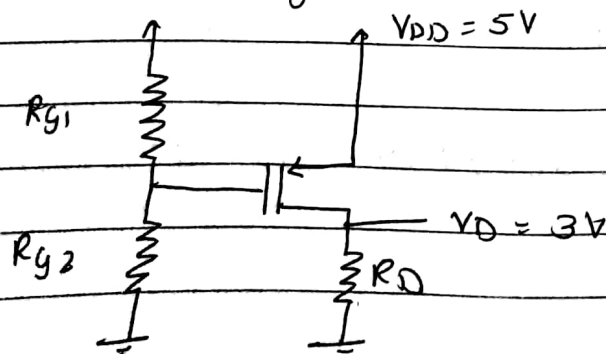

Saathi

Date / /

Saathi

$$V_S = 5V$$

$$V_D = 3V$$

$$I_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) V_{OV}^2$$

$$0.5 = \frac{1}{2} \times 10^{-3} V_{OV}^2$$

$$V_{OV} = -1V$$

$$V_{OV} = V_{GS} - V_{thp}$$

$$V_{GS} = V_G - V_S$$

$$V_G = -2 + 5$$

$$V_G = 3V$$

$$R_D = \frac{V_D}{I_D} = \frac{3}{0.5} = 6 k\Omega$$

$$V_G = \frac{V_{DD} \cdot R_{G12}}{R_{G11} + R_{G12}}$$

$$3 = \frac{5(R_{G12})}{R_{G11} + R_{G12}}$$

$$3R_{G11} + 3R_{G12} = 5R_{G12}$$

$$3R_{G11} = 2R_{G12}$$

$$R_{G11} = 2M\Omega$$

$$R_{G12} = 3M\Omega$$

$$V_{GD} > V_t$$

$$V_G - V_D = -1$$

$$V_{D(max)} = 4V$$

$$R_{D(max)} = \frac{4}{0.5mA}$$

$$= 8 k\Omega$$


Saathi

Date ___/___/___

ii) Let Q_1 and Q_2 MOSFET, let $V_t = 0$
 $\mu_n C_{ox} = 200 \mu A/V^2$, $l_1 = l_2 = 0.8 \mu m$,
 $w_1 = 8 \mu m$ and $\lambda = 0$

i) Find the value of R_{D1} to establish current of 0.2 mA in Q_1 .

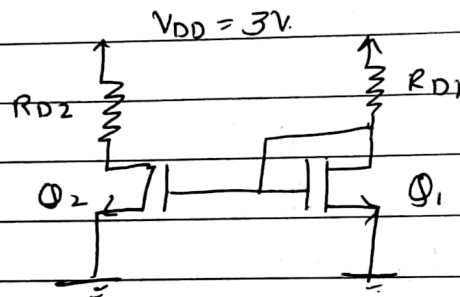ii) Find w_2 and the value of R_{D2} so that Q_2 operates in satⁿ region with $I_{D2} = 0.5 \text{ mA}$ and $V_{D2} = 1 \text{ V}$.



Sol: since $V_{GD} = 0$ and $V_{GD} < V_t$

Q_1 is in saturation region

$$I_{D1} = \frac{1}{2} k'_n \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$$

$$0.2 \times 10^{-3} = \frac{1}{2} \times 200 \times 10^{-6} \left(\frac{8}{0.8}\right) (V_{GS} - 0.6)^2$$

$$V_{GS} = 1.047 \text{ V}$$

$$R_{D1} = \frac{V_{DD} - V_{GS}}{I_D}$$

$$I_D$$

$$= \frac{3 - 1.047}{0.2 \times 10^{-3}}$$

$$= 9.765 \text{ K}\Omega$$

$$= 9.765 \text{ K}\Omega$$

Date / /

Saathi

ii) for Q_2

$$I_{D2} = 0.5 \text{ mA}$$

$$V_{D2} = 1 \text{ V}$$

$$R_{D2} = \frac{V_{DD} - V_{D2}}{I_{D2}}$$


$$= \frac{3 - 1}{0.5 \text{ mA}}$$

$$R_{D2} = 4 \text{ k}\Omega$$

$$I_{D2} = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$W_2 = 20.6 \times 10^{-6} \text{ m}$$

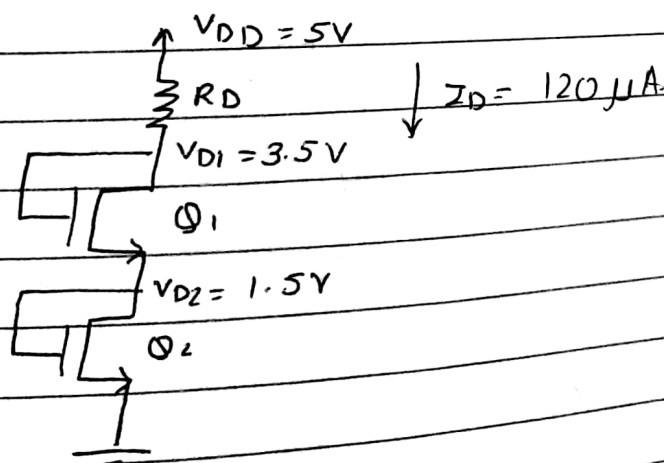2) N-mos transistor used in fig has $V_{DD} = 5 \text{ V}$, $V_t = 1 \text{ V}$, $\mu_n C_{ox} = 120 \mu$, $\lambda = 0$, $l_1 = l_2 = 1 \mu\text{m}$. Find the required values of gate width for each Q_1 and Q_2



$$V_{GS2} = V_G - V_S$$

$$= 1.5 \text{ V}$$

$$V_{GS1} = 3.5 - 1.5$$

$$= 2 \text{ V}$$

Saathi

Date ____ / ____ / ____

$$R_D = \frac{V_{DD} - V_{D1}}{I_D}$$

$$= \frac{5 - 3.5}{120 \times 10^{-6}}$$

$$= 12.5 \text{ k}\Omega$$

$$I_{D1} = \frac{k'}{2} \left(\frac{W_1}{L} \right) (V_{GS1} - V_t)^2$$


$$120 \times 10^{-6} = \frac{120 \times 10^{-6}}{2} \left(\frac{W_1}{10^{-6}} \right) (2 - 1)^2$$

$$W_1 = 2 \mu\text{m}$$

$$20 \times 10^{-6} = \frac{1}{2} \times 120 \times 10^{-6} \left(\frac{W_2}{10^{-6}} \right) (1.5 - 1)^2$$

$$W_2 = 8 \mu\text{m}$$

13)

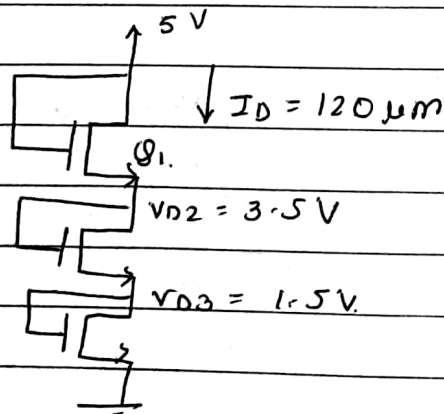

Sol: $V_{GS(3)} = 1.5 \text{ V}$

$$V_{GS(2)} = 3.5 - 1.5$$

$$= 2 \text{ V}$$

$$V_{GS(1)} = 5 - 3.5$$

$$= 1.5 \text{ V}$$

Saathi

Date / /


Saathi

$$W_1 = 8 \mu\text{m}$$

$$W_2 = 2 \mu\text{m}$$

$$W_3 = 8 \mu\text{m}$$

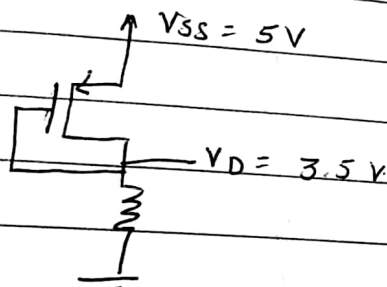4) p-mos transistor shown in fig, has $V_t = -0.7\text{V}$, $\mu_p C_{ox} = 60 \mu\text{A/V}^2$, $l = 0.8 \mu\text{m}$ and $\lambda = 0$. Determine W , R in order to establish $I_D = 115 \mu\text{A}$ and $V_D = 3.5\text{V}$.



$$V_{gs} = V_g - V_s$$

$$= -1.5\text{V}$$

$$V_{ds} = V_D - V_S$$

$$= -1.5\text{V}$$

$$R_D = \frac{V_D}{I_D}$$

$$= \frac{115 \times 10^{-6}}{30.434 \mu\text{A}}$$

MOS is in saturation region
as $V_{gd} > V_t$

$$I_D = \frac{1}{2} \frac{\mu_p C_{ox}}{l} \left(\frac{W}{l} \right) (-2.2)^2$$

$$W = \frac{115 \times 10^{-6} \times 2 \times 0.8 \times 10^{-6}}{60 \times 10^{-6} \times (-2.2)^2}$$



$$= 6.336 \times 10^{-7}$$

Date ____ / ____ / ____

MOS characteristics

$$V_{DS} = V_{DD} - I_D R_D$$

load line equation

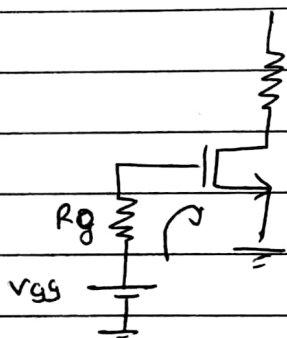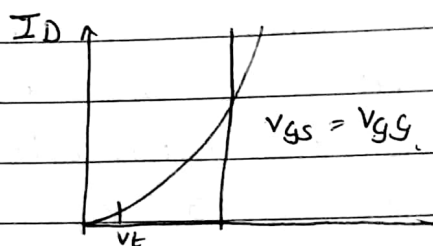


$$V_{GG} - I_g R_g = V_{GS}$$

$$I_g = 0$$

$$V_{GS} = V_{GG}$$

801

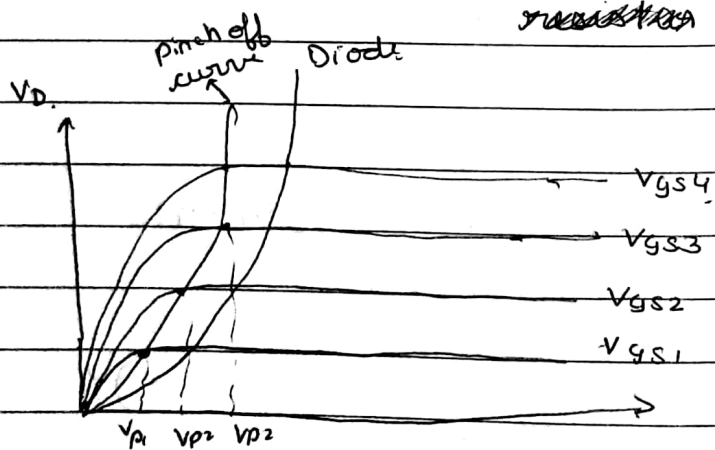$R_g \rightarrow$ just act as ~~resistor~~ short circuit




$$V_{DS} = V_{GS}$$

$$V_{GS} > V_P$$

Date ___/___/___

Saathi

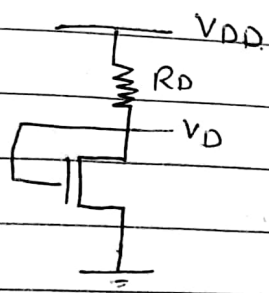For n-mos transistor shown in below fig, $V_t = 0.8V$, $V_D = 1.6V$, $I_D = 0.5mA$, neglect channel length modulation, if V_D is adjusted to $2V$ by changing the value of R & V_{DD} , find the new value of I_D



$$I_D = \frac{1}{2} K'_n \left(\frac{W}{L} \right) \left(\frac{V_{GS} - V_t}{2} \right)^2 (1 + \lambda V_{DS})$$

$$\lambda = 0$$

$$I_D = \frac{1}{2} \times K'_n \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$V_{GS1} = V_{DS1} = 1.6V$$

$$I_{D1} = 0.5mA$$

$$V_{GS2} = V_{DS2} = 2V$$

$$I_{D2} = ?$$

$$I_{D1} = \frac{1}{2} \times K'_n \left(\frac{W}{L} \right) \frac{(1.6 - 0.8)^2}{2}$$

$$0.5 \times 10^{-3} \times 2 \times \frac{1}{2} = K'_n \left(\frac{W}{L} \right)$$

$$(0.8)^2$$

$$= K'_n \left(\frac{W}{L} \right)$$

Date ____/____/____


$$I_{D2} = \frac{1}{2} \times \frac{1.56}{20000} \times 10^{-3} (2 - 0.8)^2$$

$$= 2.25 \times 10^{-3} \text{ A}$$

$$= 2.25 \text{ mA}$$

$$= 1.12 \text{ mA}$$

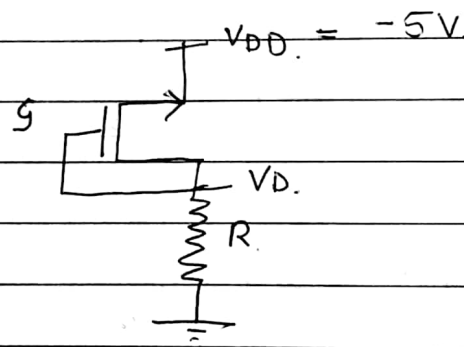- 2) The mos transistor shown in figure below has $V_t = 0.7 \text{ V}$, $k'_n = 60 \mu\text{A/V}^2$, $l = 0.8 \mu\text{m}$ and $W = 10 \mu\text{m}$ find the value of W and R in order to establish $I_D = 115 \mu\text{A}$ and $V_D = 3.5 \text{ V}$.



Sol: Given :- $V_t = 0.7 \text{ V}$ $k'_n = 60 \mu\text{A/V}^2$
 $l = 0.8 \mu\text{m}$
 $I_D = 115 \mu\text{A}$
 $V_D = 3.5 \text{ V}$

$$V_D = I_D R$$

$$3.5 = (115 \times 10^{-6}) R$$

$$R = \frac{3.5}{115 \times 10^{-6}}$$

$$= 30.434 \text{ K } \Omega$$

Saathi

Date ___/___/___

Saathi

$$V_D = V_G = 3.5 \text{ V}$$

$$V_S = -5 \text{ V}$$


$$V_{DS} = 3.5 + 5 \\ = 8.5 \text{ V}$$

$$V_{GS} = 8.5 \text{ V}$$

$$I_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (V_{GS} - V_{th})^2$$

$$W = \frac{115 \times 10^{-6} \times 2 \times 0.8 \times 10^{-6}}{60 \times 10^{-6} (8.5 - 0.7)^2} \\ = 5.04 \times 10^{-8} \text{ m}$$

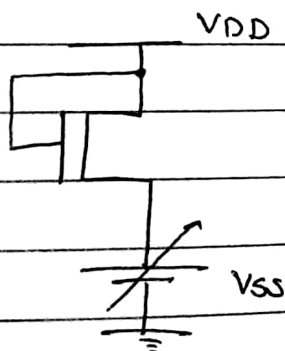For the n-mos shown in the circuit below, $V_{th} > 0$ and V_{SS} is varied from 0 to V_{DD} . Neglecting channel length modulation, Represent the function of drain current w.r.t V_{SS} .



MOS is in saturation region

Assume $V_{DD} = 3.3 \text{ V}$

Case 1: $V_{SS} = 0$

$$V_D = V_{DD}$$

$$G = V_{DD}$$


$$V_S = V_{SS}$$

Date ___/___/___

$$V_s = 0$$

$$V_{DS} = V_{DD}$$

$$V_{GS} = V_{DD}$$

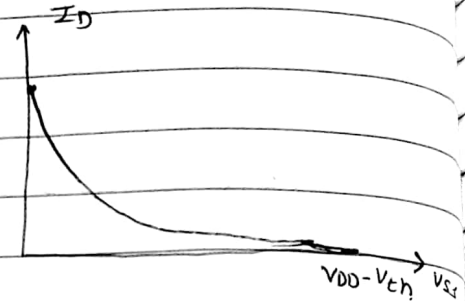

(ii) case $V_{SS} = 0.5$


$$V_{DS} = V_{DD} - V_{SS}$$

$$V_{GS} = V_{DD} - V_{SS}$$

$I_D \downarrow$

47. It is required to design the circuit shown below to operate at a dc current of 0.5 mA. Assume $V_{DD} = 5V$, $K'_n (\frac{W}{L}) = 1 \text{ mA/V}^2$, $V_t = 1V$ and $\lambda = 0$.

57.

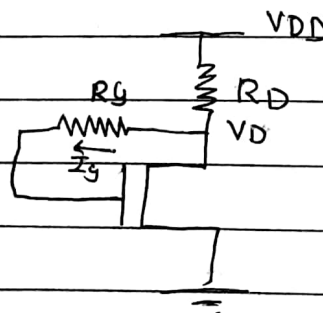

Sol: $V_{DD} = 5V$

$$I_D = \frac{1}{2} K'_n \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$$

$$\frac{0.5 \times 10^{-3} \times 2}{1 \times 10^{-3}} = (V_{GS} - V_t)^2$$

$$1 = (V_{GS} - 1)^2$$

$$2 = V_{GS}$$

Date / /

$$V_g = 2V$$

$$V_D = 2V$$

$I_g = 0$ because of high impedance

$$V_{DD} - I_D R_D = V_D$$

$$\frac{V_{DD} - V_D}{I_D} = R_D$$

$$\frac{5 - 2}{0.5 \times 10^{-3}} = R_D$$





$$30 \times 10^3 \approx R_D$$

$$\frac{30 \times 10^3}{5} = R_D$$

$$R_D = 6 k\Omega$$

5) For each of the following circuit find the labelled node voltages for all transistor. $k_n(\frac{W}{L}) = 0.4 mA/V^2$

$$V_t = 1V \text{ and } \lambda = 0$$

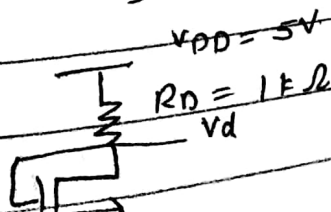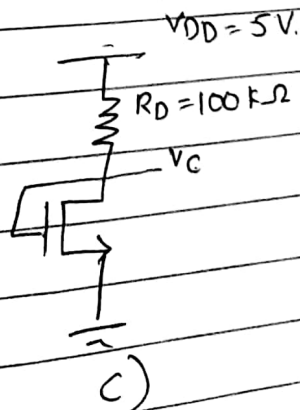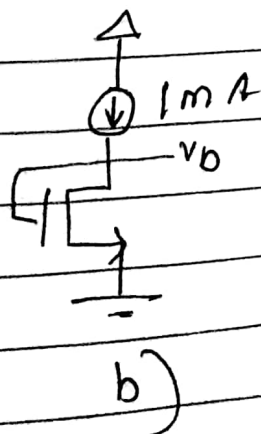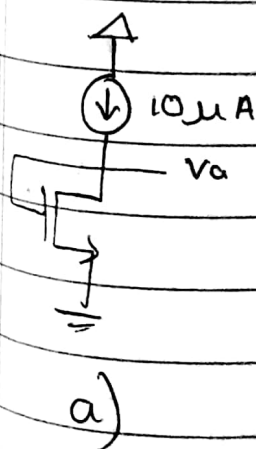

Date ____ / ____ / ____

801. Figure a:-

$$V_g = V_D = V_{GS}$$

$$I_D = \frac{1}{2} \mu_n \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$10 \times 10^{-6} = \frac{1}{2} \times 0.4 \times 10^{-3} (V_a - V_t)^2$$

$$V_a = 1.2236 \text{ V.}$$

⇒ Figure b.

$$V_D = \sqrt{\frac{2 \times 1 \times 10^{-8}}{0.4 \times 10^{-3}}} + V_t$$

$$= 3.2360 \text{ V.}$$

⇒ Figure c.

$$V_{DD} - I_D R_D = V_D$$

$$V_{DD} - I_D R_D = V_{GS}$$

$$5 - I_D (100 \times 10^3) = V_{GS}$$

$$I_D = \frac{1}{2} \times 0.4 \times 10^{-3} (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 0.4 \times 10^{-3} (5 - I_D (10^5) - 1)^2$$

$$= 0.2 \times 10^{-3} (4 - I_D (10^5))^2$$

$$= 0.2 \times 10^{-3} (16 + 10^{10} I_D^2 - 2(4) I_D 10^5)$$

$$I_D = 3.2 \times 10^{-3} + 0.2 \times 10^7 I_D^2 - 1.6 \times 10^2 I_D$$

$$3.2 \times 10^{-3} + 0.2 \times 10^7 I_D^2 - 1.6 I_D = 0$$

Date ___/___/___

Saathi

$$I_{D1} = 4.47 \times 10^{-5}$$

$$I_{D2} = 3.5 \times 10^{-5}$$

$$\begin{aligned} V_C &= V_{DD} - I_{D1} R_D \\ &= 5 - (4.47) \times 10^{-5} (100 \times 10^3) \\ &= 0.53 \end{aligned}$$

$$\begin{aligned} V_C &= V_{DD} - 3.5 \\ &= 5 - 3.5 \end{aligned}$$

$$V_C = 1.5$$

$$V_G = 1.5$$

$$V_G > V_T$$

$$\therefore \boxed{V_G = 1.5 \text{ V}}$$

$$\Rightarrow V_{DD} - I_D R_D = V_{GS}$$

$$5 - I_D (10^3) = V_{GS}$$

$$I_D = \frac{1}{2} \times 0.4 \times 10^{-3} (5 - I_D (10^3) - 1)^2$$

$$= 0.2 \times 10^{-3} (4 - 10^3 I_D)^2$$

$$= 0.2 \times 10^{-3} (16 + 10^6 I_D^2 - 8 \times 10^3 I_D)$$

$$= 3.2 \times 10^{-3} + 0.2 \times 10^{-3} I_D^2 - 1.6 I_D$$

$$0 = 3.2 \times 10^{-3} + 0.2 \times 10^{-3} I_D^2 - 1.6 I_D$$

$$I_{D1} = 0.012$$


~~I_{D2}~~

$$V_{C1} = -7$$

$$V_{C2} =$$

Page No.

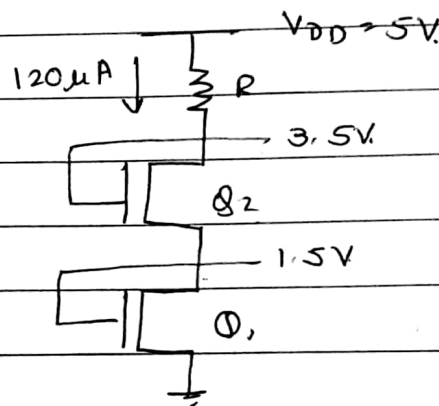67. The n-mos transistor show below,
 $V_t = 1V$, $\mu_n C_{ox} = 120 \mu A/V^2$, $l_1 = l_2 = 1 \mu m$
 Find the required value of gate widths for Q_1 and Q_2 and also find the value of R .



Sol: $V_{G1} = V_{D1} = V_{GS1} = V_{DS1} = 1.5V$

$V_{G2} = 3.5V = V_{D2}$

$V_{S2} = 1.5V$

$V_{GS2} = 2V$

$$\frac{120 \times 10^{-6}}{1} = \frac{1}{2} \frac{(W/L)_2}{(W/L)_1} \frac{(V_{GS2} - V_t)^2}{(V_{GS1} - V_t)^2} \times \mu_n C_{ox}$$

~~(K_n)~~

$$120 \times 10^{-6} = \frac{1}{2} \times \frac{W_1}{10^{-6}} \frac{(1.5 - 1)^2}{(0.5)^2} \times 120 \times 10^{-6}$$

$$\frac{2 \times 10^{-6}}{(0.5)^2} = W_1$$

$$W_1 = 8 \mu m$$

Saathi

Date / /

Saathi

$$120 \times 10^{-6} = \frac{1}{2} \frac{\mu_2}{10^{-6}} \times 120 \times 10^{-6} (2-1)^2$$

$$2 \mu\text{m} = \mu_2$$


$$\mu_2 = 2 \mu\text{m}$$

$$R = \frac{V_{DD} - V_D}{I_D} = \frac{5 - 3.5}{120 \times 10^{-6}}$$

$$R = 12.5 \text{ K}\Omega$$

below,
 $l_2 = 1 \mu\text{m}$
gate
also

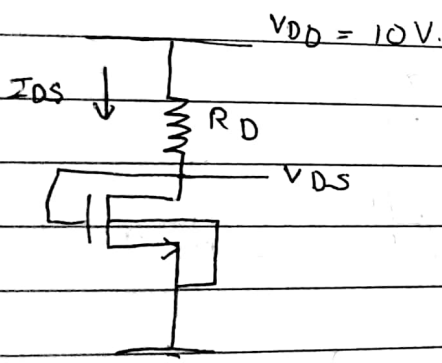7) Given a n-mos circuit, $V_{DD} = 10\text{V}$,
 $\mu_n C_{ox} = 10^{-4} \text{ A/V}^2$, $V_t = 1\text{V}$, $I_{DS} = 0.5\text{mA}$
Evaluate V_{DS} and R_D .



Assume $\mu/L = 1$

R_D

$$I_D = \frac{1}{2} \times \mu_n C_{ox} \left(\frac{\mu}{L}\right) (V_{GS} - V_t)^2$$

$$0.5 \times 10^{-3} = \frac{1}{2} \times 10^{-4} \times 1 (V_{GS} - 1)^2$$

$$\frac{10^{-3}}{10^{-4}} = (V_{GS} - 1)^2$$

$$\sqrt{10} = V_{GS} - 1$$

$$4.16 = V_{GS}$$

$$V_{GS} = 4.16 \text{ V}$$

Page No.



Saathi

Date ___/___/___

$$V_{DS} = 4.16 \text{ V}$$



$$V_{DD} - I_D R_D = V_{DS}$$

$$10 - (0.5 \times 10^{-3}) R_D = 4.16$$

$$R_D = 11.68 \text{ k}\Omega$$

Current Mirror Basics and
Figures of merit

current mirror

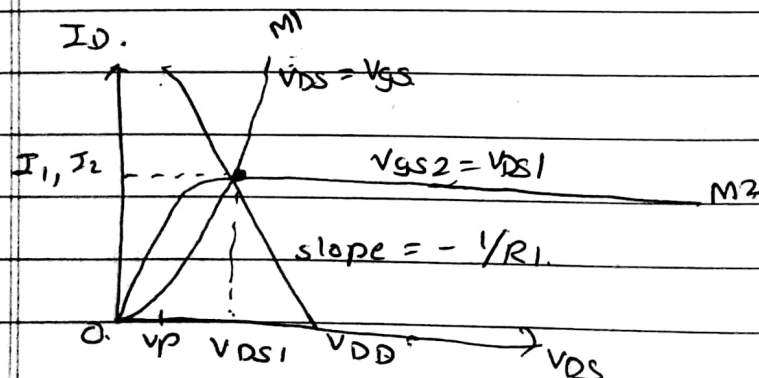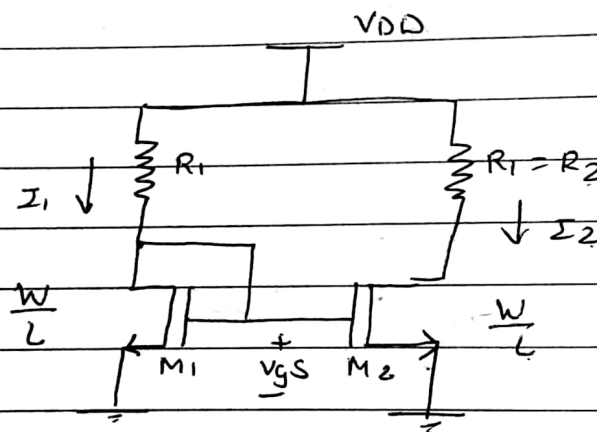

$$V_{DS1} = V_{GS}$$

$$V_{DS2} = V_{DD} - I_2 R_2$$

The entire circuit will have
only one load line




Date ___/___/___

Saathi

W/L is same


V_{GS}, V_{DS} is same

$$I_1 = I_2$$

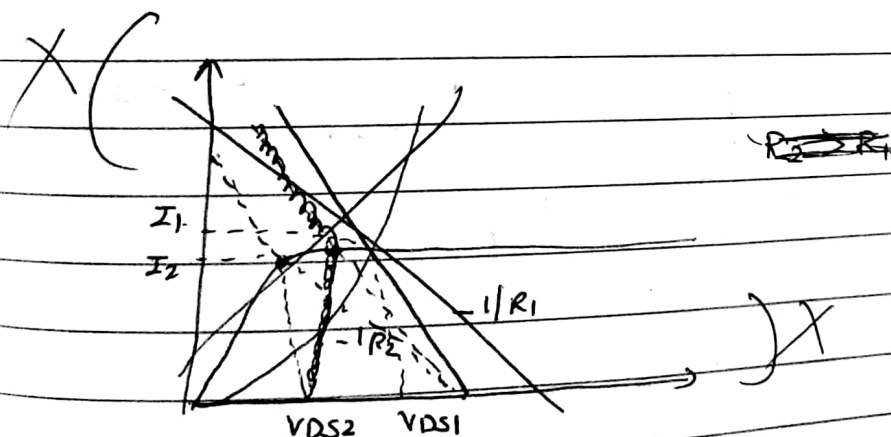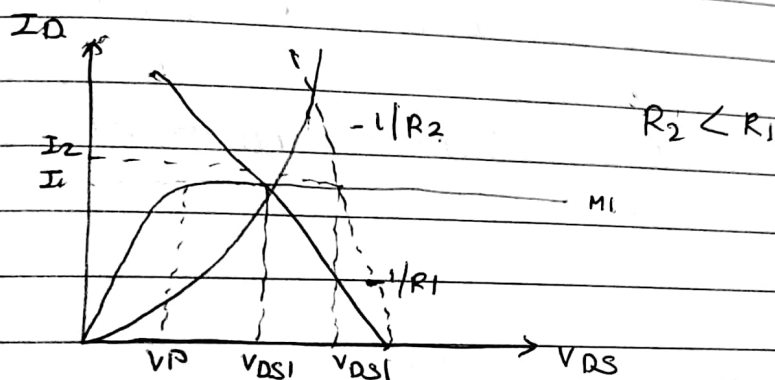
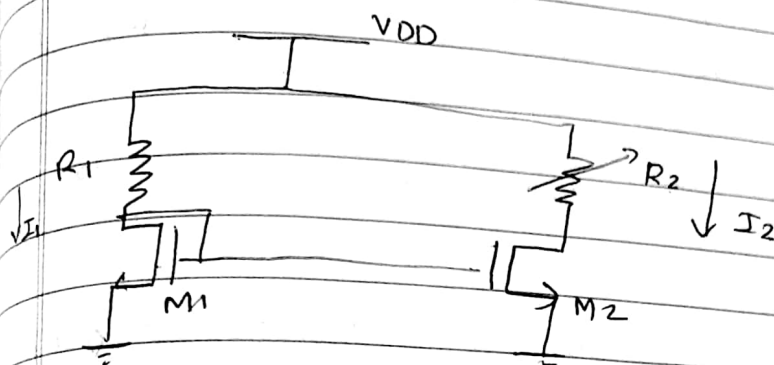


If M_2 is maintained in saturation region, there is slight change in I_2 because in saturation region, I_D doesn't depend on V_{DS} .

Date ____ / ____ / ____

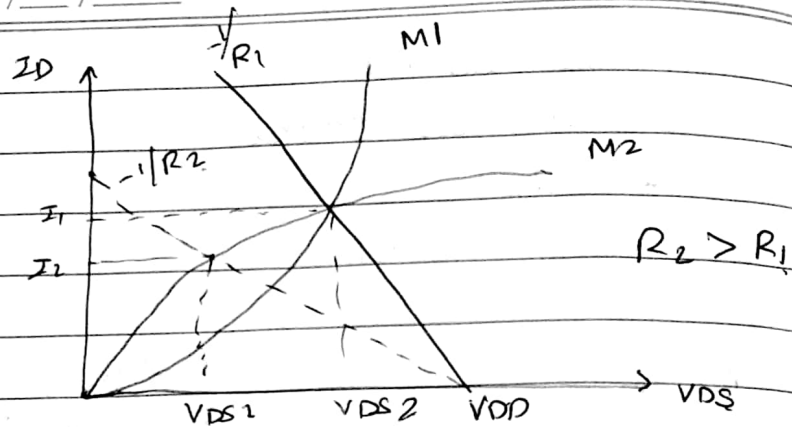

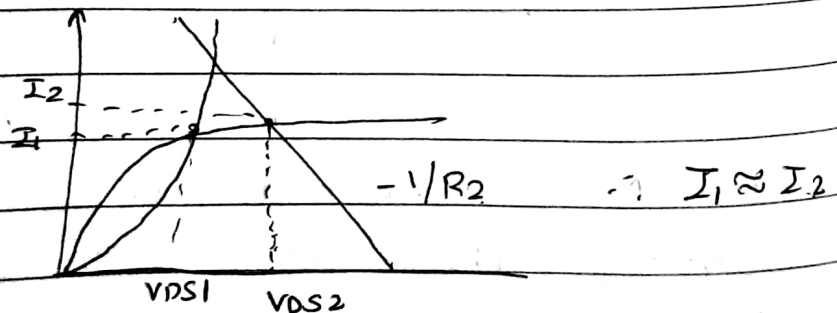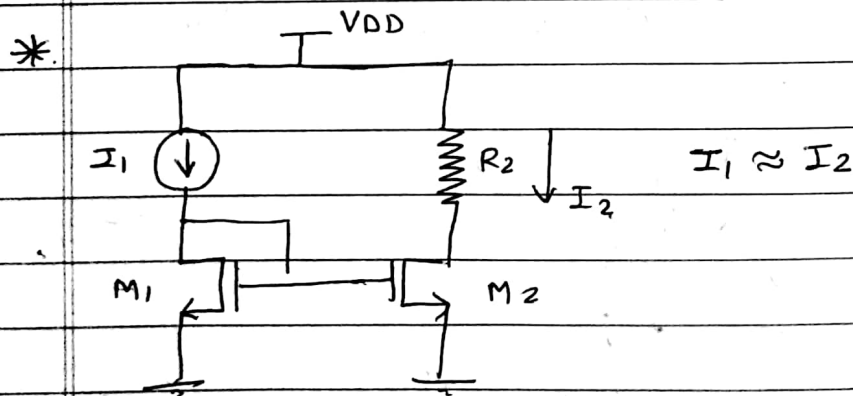Now MOS is in triode region,
 I_2 is different from I_1 .
 (difference is large), as in
 triode region, current depends
 on V_{DS} .



Saathi

Date / /

$$I_1 = f(V_{GS1}) \quad \text{--- (1)}$$

$$I_2 = f(V_{GS2}) \quad \text{--- (2)}$$

$$V_{GS1} = V_{GS2}$$

} nonlinear funⁿ.

$$I_2 = f(V_{GS1})$$



$$V_{GS1} = f^{-1}(I_1) \rightarrow \text{inverse nonlinear fun}^n.$$

$$I_2 = f(f^{-1}(I_1))$$

$$\boxed{I_2 = I_1} \rightarrow \text{linear fun}^n$$

non-linearity is cancelled,
only linearity is present.

current source model.

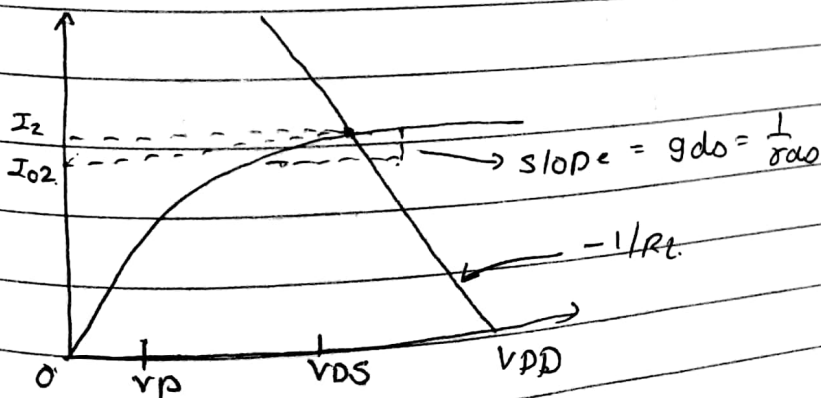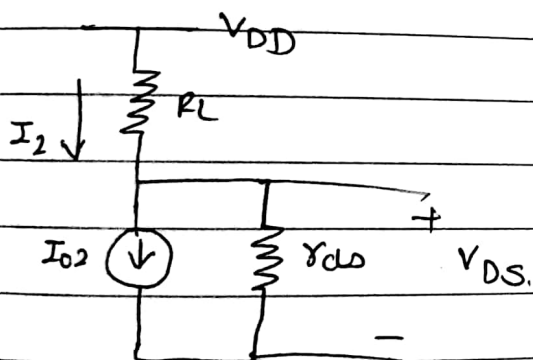

Because of r_{ds}

$$I_2 \neq I_{02}$$

Saathi

Date ____ / ____ / ____


Figure of merit :-

Ideal current source :- It is the current which does not ~~have~~ change with change in voltage drop across it.

High value of r_{ds} , make current source, ideal.

- 1) If R_o is very high, $I_o = I_{o1}$
- 2) Output swing = 0.2 ~ 5.0 V.
 (assuming $V_{GS1} = V_{GS2} = 0.7V$ (diode))
 $\therefore V_{DS2} \geq V_{GS2} - V_t$
 $= V_{DS2(min)} = 0.2$
 $V_{DS2(max)} = V_{DD} = 5V$

Derivation of Mirror Ratio:

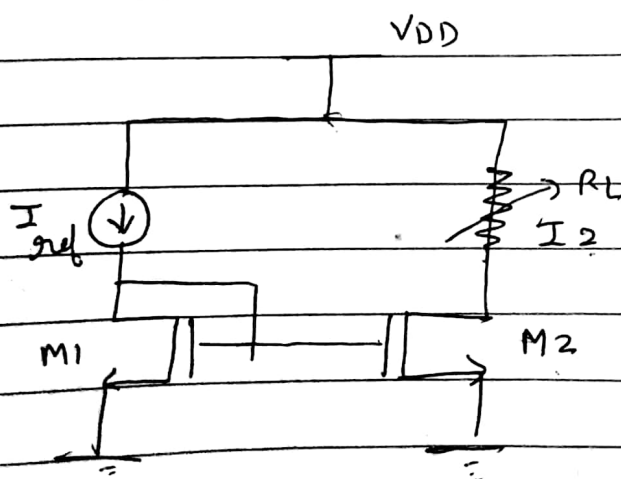

Date / /

Saathi

Case 1:- When the aspect ratio of M_1 and M_2 same $\left(\frac{W_1}{L_1} = \frac{W_2}{L_2}\right)$.

$$I_{ref} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \frac{(V_{GS1} - V_t)^2}{2} (1 + \lambda V_{DS1})$$

$$I_2 = \mu_n C_{ox} \left(\frac{W}{L}\right)_2 \frac{(V_{GS2} - V_t)^2}{2} (1 + \lambda V_{DS2})$$

MOSFETs are of the same family
 $\therefore \mu_n C_{ox}$ is same

($\because$ MOSFETs are matched).

$$V_{GS1} = V_{GS2}$$

$$\frac{I_2}{I_{ref}} = \frac{\left(\frac{W}{L}\right)_2 (1 + \lambda V_{DS2})}{\left(\frac{W}{L}\right)_1 (1 + \lambda V_{DS1})}$$

$$\therefore \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_1$$

$$I_2 = \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

$$I_{ref}$$

a) If $\lambda = 0$

$$I_2 = I_{ref}$$

b) ~~Case 2~~ When $V_{DS1} = V_{DS}$

$$I_2 = 1$$

$$I_{ref}$$

Case 2:- When aspect ratios are not matched.

$$\frac{I_2}{I_{ref}} = \frac{(W/L)_2 (1 + \lambda V_{DS2})}{(W/L)_1 (1 + \lambda V_{DS1})}$$

a) when $\lambda = 0$

$$\frac{I_2}{I_{ref}} = \frac{(W/L)_2}{(W/L)_1}$$

b) when $V_{DS2} = V_{DS1}$


$$\frac{I_2}{I_{ref}} = \frac{(W/L)_2}{(W/L)_1}$$

Problems

1) In a basic current mirror circuit shown below, Q_1 & Q_2 has $V_t = 0.6V$. $\mu_n C_{ox} = 200 \mu A/V^2$, $l_1 = l_2 = 0.8 \mu m$, $w_1 = 8 \mu m$, $\lambda = 0$

a) Find the value of R required to establish a current of $0.2mA$ in Q_1 transistor.

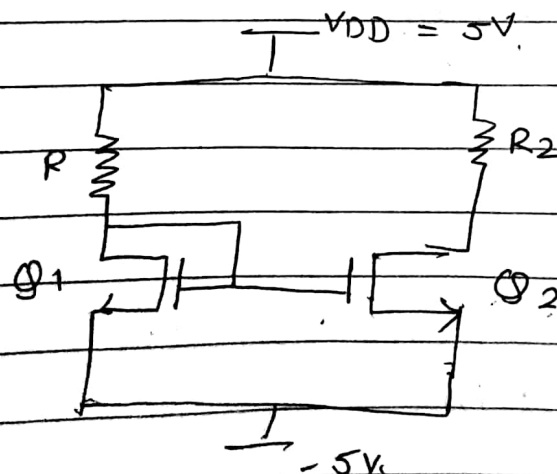b) Find w_2 and R_2 so that Q_2 operates in saturation region with $I_2 = 0.5mA$. $V_D = 1V$.



Date / /

Saathi

a) $I_{D1} = 0.2 \text{ mA}$

$$I_{D1} = \frac{1}{2} K'_n \left(\frac{W}{L} \right)_1 (V_{GS1} - V_t)^2$$

$$0.2 \times 10^{-3} = \frac{1}{2} \times 200 \times 10^{-6} \left(\frac{8}{0.8} \right) (V_{GS1} - 0.6)^2$$

$$0.2 = (V_{GS1} - 0.6)^2$$

$$V_{GS1} = 1.047 \text{ V}$$

$$V_{G1} - V_{S1} = 1.047$$

$$V_{G1} = 1.047 + 0.5$$

$$V_{G1} = \text{GND} \quad V_{S1} = V_{D1} = -3.953$$

$$V_{DD} - I_1 R = V_{G1}$$

$$5 - (0.2 \times 10^{-3}) R = -3.953$$

$$R = 44.76 \text{ k}\Omega$$

b) $V_{GS1} = 1.047 \text{ V}$

$$V_{GS2} = 1.047 \text{ V}$$

$$I_{D2} = \frac{1}{2} \times 200 \times 10^{-6} \left(\frac{W_2}{0.8 \times 10^{-4}} \right) (1.047 - 0.6)^2$$

$$\frac{0.5 \times 10^{-3} \times 2 \times 0.8}{200 \times (1.047 - 0.6)^2} = W_2$$

$$W_2 = 0.2001 \times 10^{-4} \text{ m} = 20 \mu\text{m}$$

$$I_2 R_2 - V_{DS2} - V_{SS} = 0$$

$$5 - (0.5 \times 10^{-3}) R_2 - (V_D) = 0$$


$$V_D = R_2 = 8 \text{ k}\Omega$$

Page No.

Date ____ / ____ / ____

Current Mirror Applications

1) Multiple current mirrors

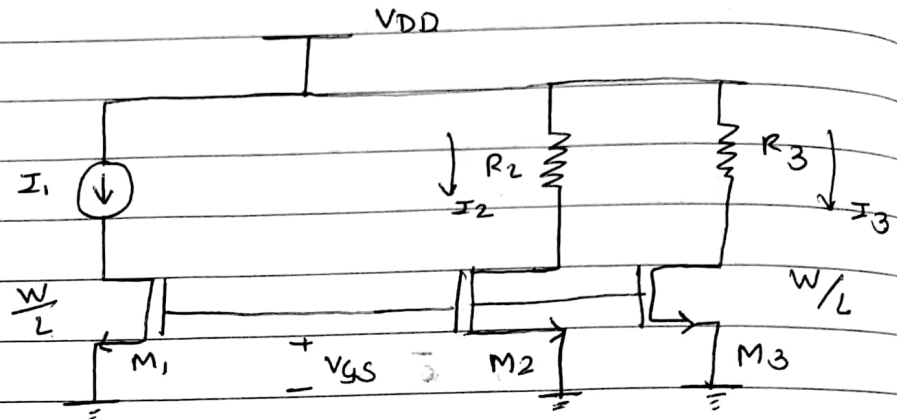

$$V_{DS,1} = V_{GS}$$

$$V_{DS,2} = V_{DD} - I_2 R_2$$

$$V_{DS,3} = V_{DD} - I_3 R_3$$

V_{GS} of all 3 are same

W/L of all 3 are same

$$\Rightarrow I_2 \approx I_1 \quad I_3 \approx I_1$$

$\Rightarrow I_2$ is not same as I_1 because V_{DS} of M_2 is not same as V_{DS} of M_1 .

$\Rightarrow$ Ensure M_2 and M_3 are in satⁿ.

2) Current mirror multiplier

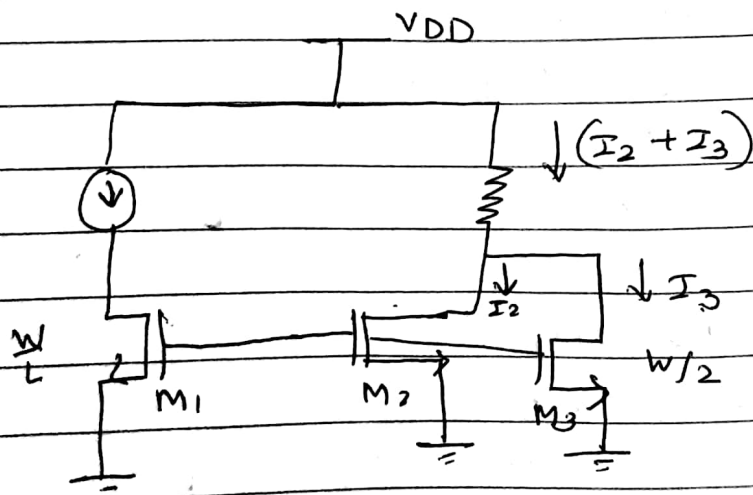


Fig 2:

In this $V_{DS2} = V_{DS3}$
 (MOSFET, when considered w.r.t vertical field,
 it acts as capacitor). M_2, M_3 are
 Date / / like capacitor. Saathi

$$V_{DS} = V_{GS}$$

$$V_{DS(2)} = V_{DD} - (I_2 + I_3)R_2$$

$I_2 = I_3$, if M_2 and M_3 are of
 same size.
 current through $R_2 = 2I_2$

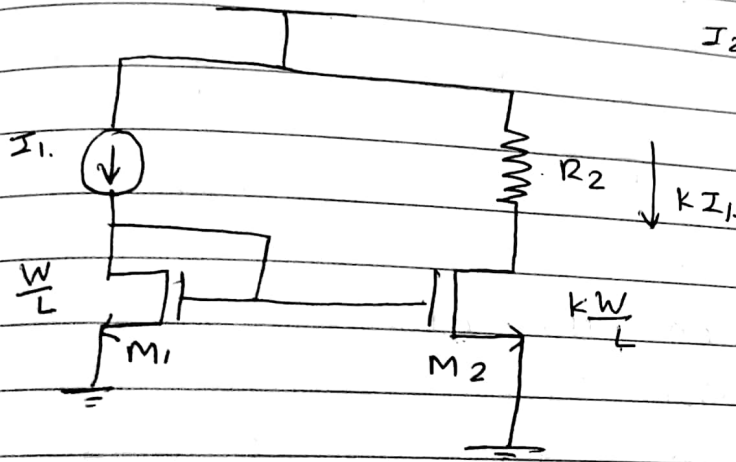


Fig 3

In fig 2, M_2, M_3 are parallel
 as gate are shorted, drains are
 shorted and source terminal is
 grounded


In fig 2, M_2, M_3 have same
 length but different width

In fig 3, the current is scaled
 Relation between I_1 & kI_1 is linear

Date ____ / ____ / ____

Saathi


Current sink and current source

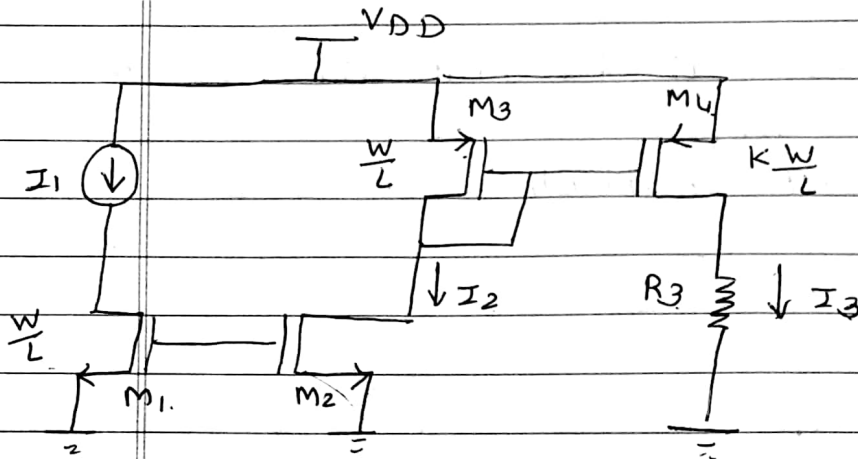


From the above figure

$$V_{GS1} = V_{GS2} \quad I_1 = I_2$$

$$V_{GS3} = V_{GS4} \quad I_3 = k I_2$$

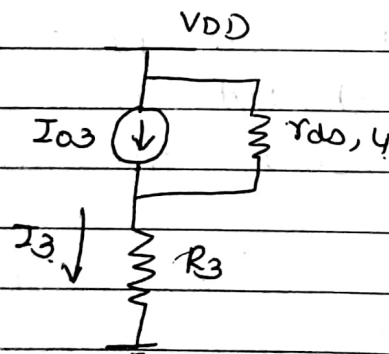

current source

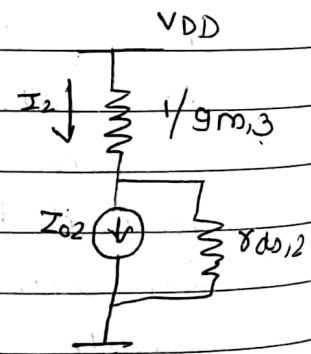

current sink

M3 is p-mos

$V_{SD3} = 0.7V$ which is very small

$\therefore$ M2 is in saturation

$\therefore$ M2 is mirror version of M1

current source $\rightarrow$ pmos (load is connected to ground)

current sink $\rightarrow$ nmos, (if mosfet is connected to V_{DD} , load is connected to ground)

Date: ___/___/___

Saathi

Saathi


Now I_2 is a current source
 M_4 is a current source

$\Rightarrow$ If M_1 and M_2 are of same size
 $\therefore I_1 = I_2$

One is current source i.e. M_4 ,
 as it is dropping current from V_{DD} and other is current sink.
 In both the circuit, the current is in downward direction

Active load


(Application of current mirror)

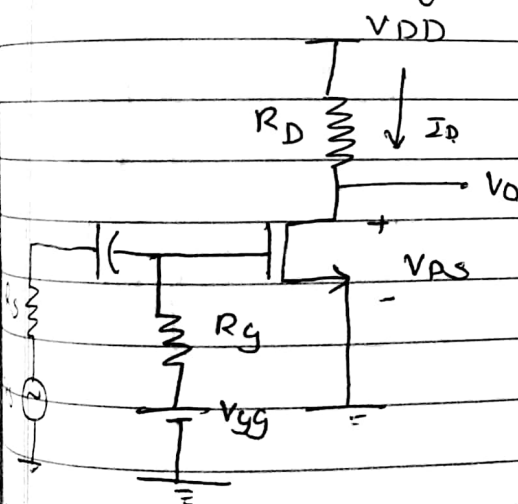

R_D is restricting factor

$$V_{DD} - I_D R_D = V_{DS}$$

$$A = -g_m R_D$$

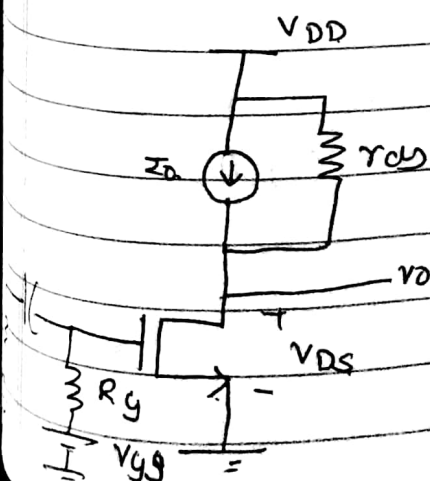

The gain will be boosted,
 if R_D will be replaced by
 current source
 and mosfet will be in saturation


Saathi

Date ____ / ____ / ____

current mirror as active load

- Diode connected MOS is fed from a well stabilized current reference
- The stability of mirrored currents depends upon stability of I_{ref}
- Active load defines Q point

Numericals

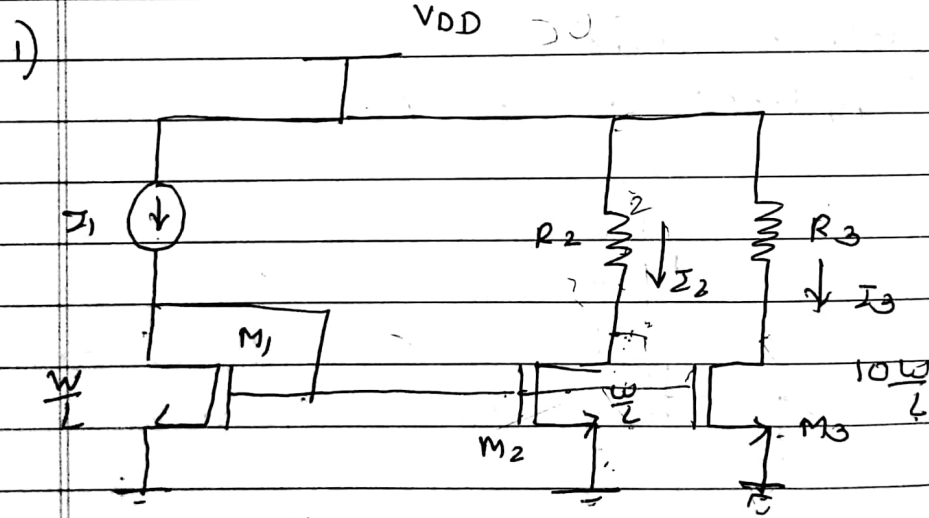

Given $V_{DD} = 5V$

$I_1 = 10 \mu A$ $R_2 = 200 k\Omega$

- i) Compute voltage across M_2
- ii) $V_{GS} = 1V$, $r_{ds} = 2 M\Omega$, I_2 ?
- iii) Compute the value of R_3 for which current in M_3 exactly $100 \mu A$

Date / /

Saathi

Assume, $I_1 = I_2$

$$I_1 = 10 \mu A$$

$$I_2 = 10 \mu A$$


(on the basis of w/L)

Voltage drop across $R_2 = 2V$
 $V_{D2} = 3V$

$\therefore M_2$ is in saturation region
 $\therefore$ our assumption is correct
 voltage across M_2 is $3V$

$$V_{GS} = 2V$$
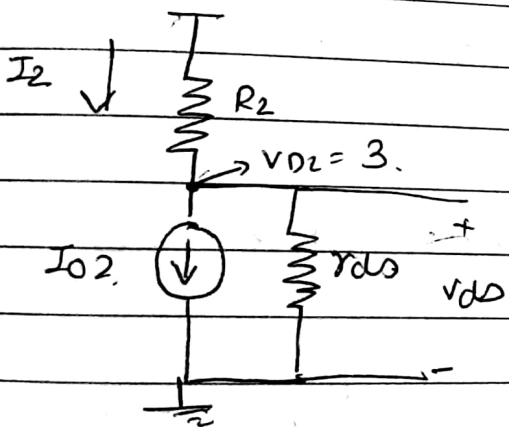
$$I_{D2} = \frac{1}{2} k'_n \left(\frac{w}{L}\right) (V_{GS} - V_t)^2$$



current across $r_{DS} = \frac{3}{r_{DS}} = 3 = 1.5 \mu A$

$$\therefore I_2 = 10 + 1.5$$

$$= 11.5 \mu A$$

$I_3 = 100 \mu A$ for exact mirroring

$$V_{DS3} = V_{DS1}$$


$$R_3 = \frac{V_{DD} - V_{DS3}}{I_3} = \frac{5 - 1}{100 \times 10^{-6}} = 4 \times 10^4 \Omega$$

$$= 40 k\Omega$$

Page No.

~~1/gm~~

Re

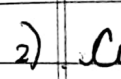

4	2
---	---

21	1
----	---








Date ___/___/___

Saathi

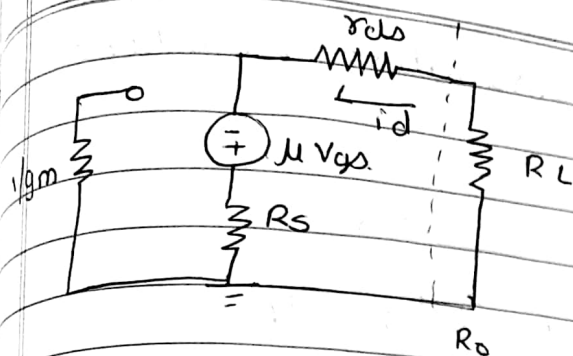

small signal model of M_2


Remove R_L , connect a voltage source
 $V_{gs} = -i_d R_s$

$$i_d = \frac{V_0 - \mu i_d R_s}{r_{ds} + R_s}$$

$$i_d (r_{ds} + R_s + \mu R_s) = V_0$$

$$R_0 = r_{ds} + R_s + \mu R_s$$

Cascode current mirror

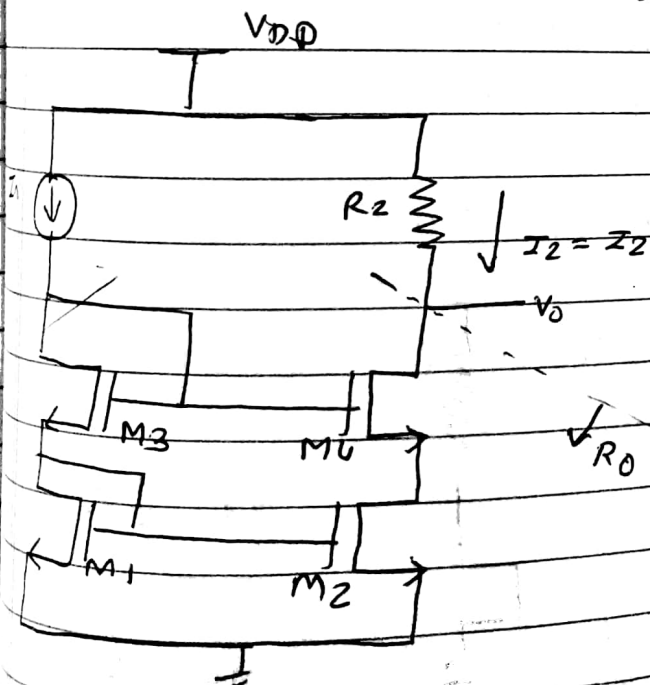


M_1, M_2 are current mirror,
 whose role is used to provide

Page No.

Date ____ / ____ / ____

source degenerative resistance

Model.

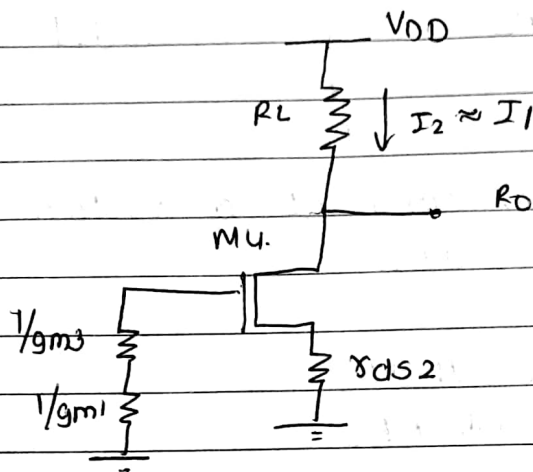

$$R_o = r_{ds4} + r_{ds2} + g_{m4} r_{ds4} r_{ds2}$$


$$R_o = (2 + \mu) r_{ds}$$

$$V_{gs1} = V_{gs} = 0.7V$$

$$V_{gs3} = V_{gs4} = 1.4V$$


Drop across $M_4 = 0.7V$

Wilson Current mirror

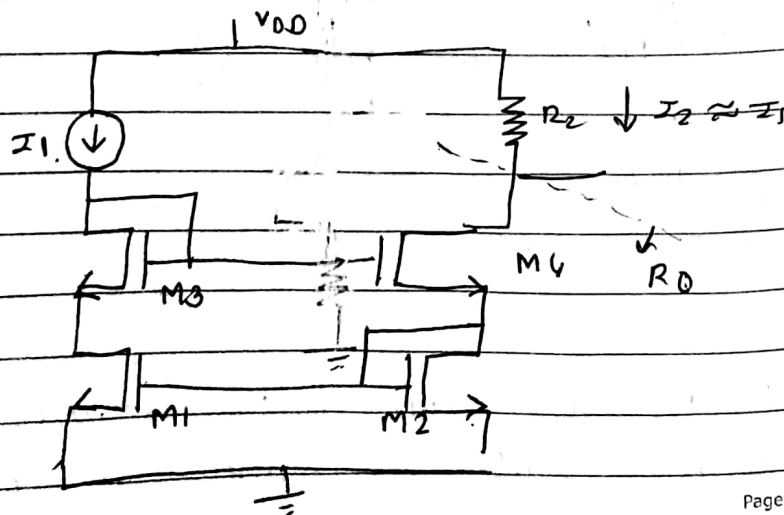


Date ___/___/___

Saathi

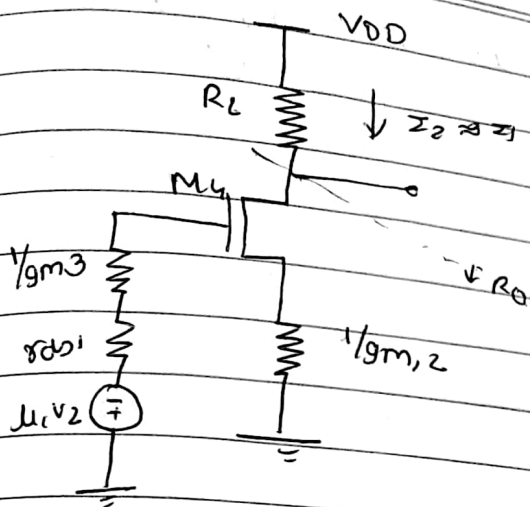

Current Mirror Basics & Figures of merit :-

Current mirror

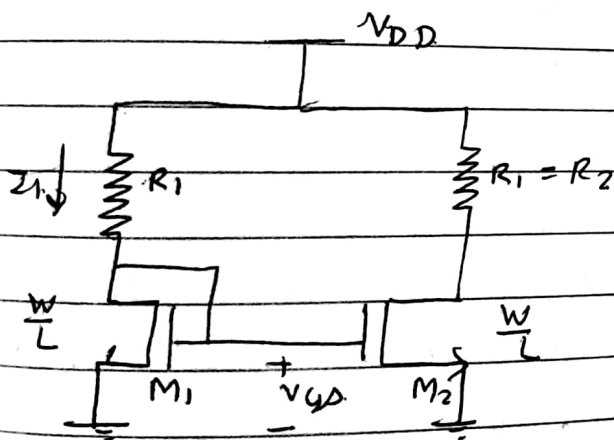

M1 is diode connected device

$$V_{DS1} = V_{GS1}$$

$$V_{GS1} = V_{GS2}$$

Case 1 :-

$$R_1 = R_2$$

$$V_{DS2} = V_{DD} - I_2 R_2$$


$$V_{DS1} = V_{DD} - I_1 R_1$$

$$V_{DS2} = V_{DS1} \Rightarrow I_1 = I_2$$


Page No.

Date ____/____/____


$\therefore I_2$ will be mirrored value of I_1

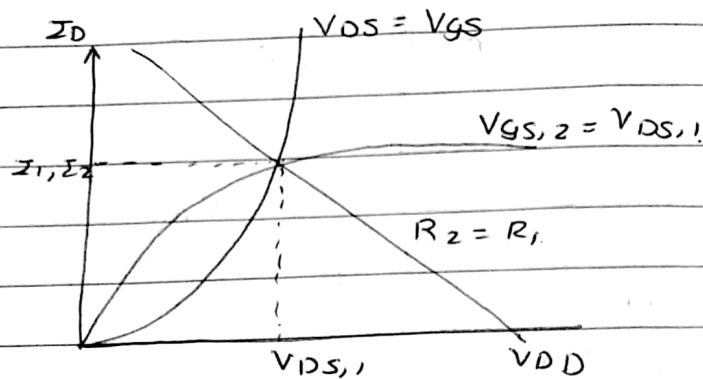

case 2 :-

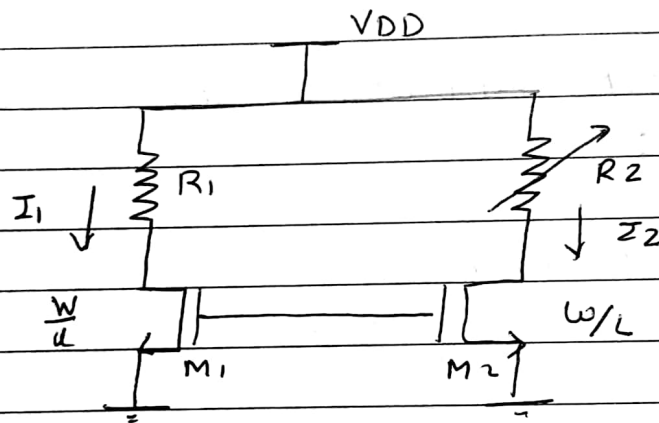

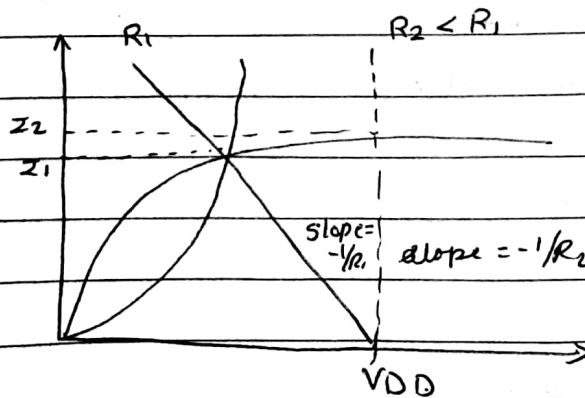→ When $R_1 \neq R_2$ and $R_2 < R_1$
The slope of load line of M_2 is larger than that of M_1 .




The device is still in saturation region and $I_1 \approx I_2$

Date ___/___/___


Saathi

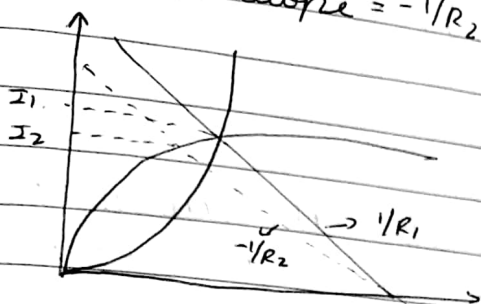when $R_2 > R_1$, slope $= -1/R_2$ decreases



In this case, the mosfet will be in saturation region.

Current source model

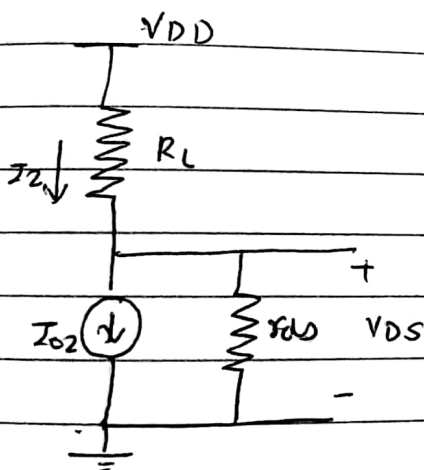

The characteristic line in saturation region has a slope $1/r_{ds}$

$$I_2 \neq I_{02}$$

$$I_2 = I_{02} + \frac{V_{ds}}{r_{ds}}$$

Figures of merit

The current source has 2 performance parameters

The R_o which accounts for the load current variation with R_L .

Page No.

Date ____ / ____ / ____


The o/p voltage during

Q) Calculate the o/p current I_o , for the basic current mirror, if $k'_n = 250 \mu A/V^2$, $V_t = 1V$, $V_{DD} = 10V$, $\lambda = 0.0133/V$, $I_{ref} = 150 \mu A$, $V_{DS} = 10V$.

Sol:-

$$V_{DS} = V_{GS1} = V_{GS2} = 10V$$

$$I_{ref} = 150 \mu A$$

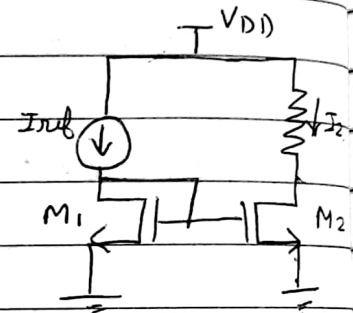

$$V_{DS2} = V_{GS2} = 10V$$

$$= 10V$$

$$V_{DS2} = 10V$$

$$= 10V$$

(min)

assume $(\frac{W}{L})_1 = (\frac{W}{L})_2$

$$\frac{I_o}{I_{ref}} = \frac{(\frac{W}{L})_2 (1 + \lambda V_{DS2})}{(\frac{W}{L})_1 (1 + \lambda V_{DS1})}$$

$$\frac{I_o}{I_{ref}} = \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

$$I_{ref} = \frac{1}{2} \times 250 \times 10^{-6} (V_{GS1} - 1)^2 \left[\begin{array}{l} (1 + \lambda V_{DS}) \\ \text{is not} \\ \text{considered} \\ \text{as it's} \\ \text{very small} \end{array} \right]$$

$$\sqrt{\frac{150 \times 2}{250}} = V_{GS1} - 1$$

$$V_{GS1} = 2.095 V = V_{DS1}$$

Date ___/___/___


Saathi

$$I_0 = (150 \times 10^{-6}) \left(1 + \frac{(0.0133)(10)}{1 + (0.0133)(2.095)} \right)$$

$$I_0 = 165.34 \mu A$$

the
= 250 μA
33 / V.

VDD

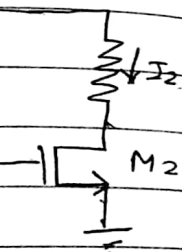

calculate the mirror ratio for a mos current mirror.

a) $\lambda = 0$

b) $\lambda = 0.02 V^{-1}$

given $V_t = 1V$, $k'_n = 25 \mu A/V^2$,
 $I_{ref} = 50 \mu A$, $V_{DS2} = 10V$.

a) aspect ratio of $M_2 = 25/1$

aspect ratio of $M_1 = 3/1$

c) " " " $M_2 = 2/1$

" " " $M_1 = 5/1$

a) considering $\lambda = 0$

i) $(w/L)_2 = 25/1$ & $(w/L)_1 = 3/1$

$$\frac{I_0}{I_{ref}} = \frac{(w/L)_2}{(w/L)_1} = \frac{25/1}{3/1} = \frac{25}{3} = 8.33$$

(if λ was)
is not
considered
as it's
very small

ii) $(w/L)_2 = 2/1$ & $(w/L)_1 = 5/1$

$$\frac{I_0}{I_{ref}} = \frac{2/1}{5/1} = \frac{2}{5} = 0.4$$

b) considering $\lambda = 0.02 V^{-1}$

$$I_{ref} = 50 \mu A$$

$$50 \times 10^{-6} = 1 \times 25 \times 10^{-6} \times \frac{3}{1} (V_{GS} - V_t)^2$$

Page No.

Saathi

Date ___ / ___ / ___

$$V_{GS1} = 2.15 \text{ V} = V_{DS1}$$

$$\begin{aligned} \frac{I_0}{I_{ref}} &= \frac{(\mu/L)_2 (1 + \lambda V_{DS2})}{(\mu/L)_1 (1 + \lambda V_{DS1})} \\ &= \frac{(25/1) (1 + (0.02)(10))}{(3/1) (1 + (0.02)(2.15))} \\ &= 9.58 \end{aligned}$$

$$\text{ii) } I_{ref} = \frac{1}{2} \times 25 \times 10^{-6} \times \frac{5}{1} (V_{GS1} - V_t)^2$$

$$0.89 = V_{GS1} - V_t$$

$$V_{GS1} = 1.89 \text{ V.}$$

$$\begin{aligned} \frac{I_0}{I_{ref}} &= \frac{(2/1) (1 + (0.02)(10))}{(5/1) (1 + (0.02)(1.89))} \\ &= 0.4628 \end{aligned}$$

Q) Calculate the mirror ratio when $V_{GS} = 2 \text{ V}$, $V_A = 50 \text{ V}$, $V_{DS2} = 1 \text{ V}$.


Q) Calculate the mirror ratio when $V_{GS} = 2.5 \text{ V}$, $\lambda = 0.01 \text{ /V}$, $V_{DS2} = 10 \text{ V}$ & $(\mu/L)_2 = 20$ & $(\mu/L)_1 = 10$.

Date / /

Saathi

Current Mirror Topologies

small signal model of current mirror

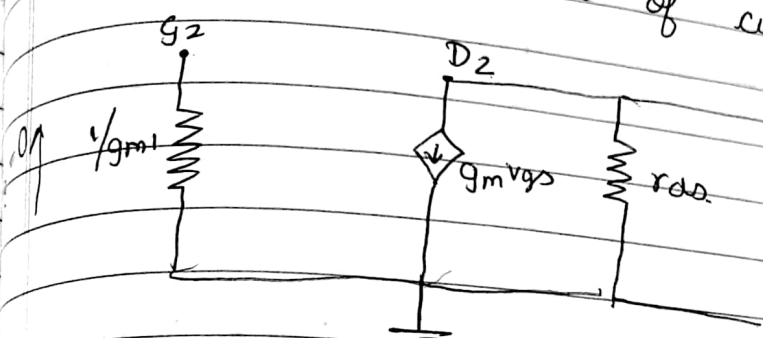


drop across $1/g_{m1} = 0$

$$\therefore V_s = 0$$

$$\therefore V_{gs} = 0$$

output resistance = r_{ds}

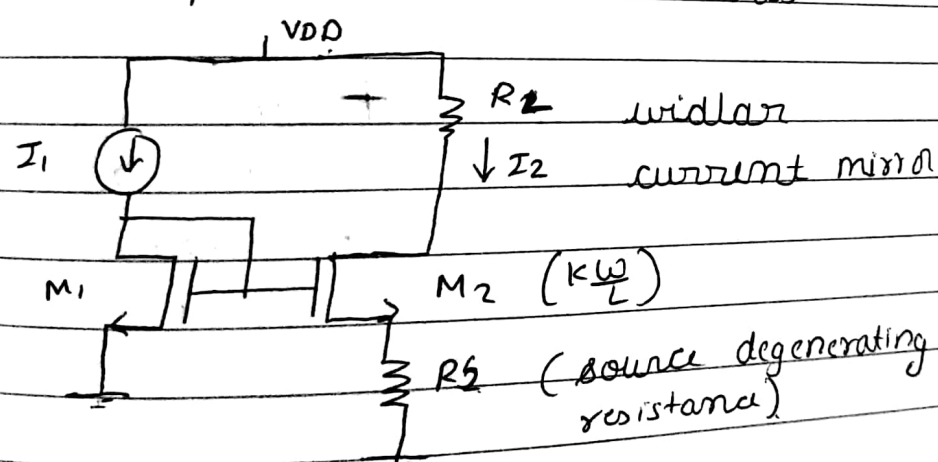

$$V_{gs1} = V_{gs2} + I_2 R_S$$

$$V_{gs2} = (V_{gs1} - I_2 R_S)$$

$$\therefore V_{gs2} < V_{gs1}$$


$$I_2 < I_1$$

in order to make I_2 same as I_1

$$(W/L)_2 = K (W/L)_1$$

Date ____ / ____ / ____

Saathi

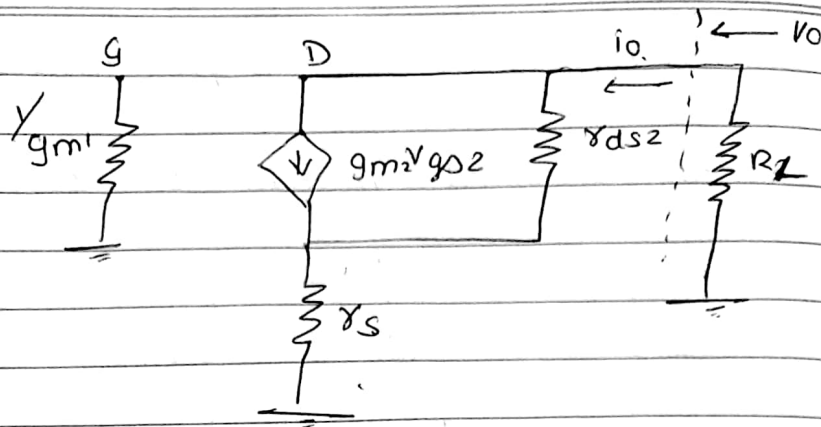

$$V_o - i_o r_{ds2} + g_m V_{gs2} r_{ds2} - i_o r_s = 0$$

$$i_o = \frac{+g_m V_{gs2} r_{ds2} + V_o}{r_{ds2} + r_s}$$

$$i_o = \frac{+g_m V_{gs2} r_{ds2} + V_o}{r_{ds2} + r_s}$$

$$i_o = \frac{V_o + g_m r_{ds2} (V_{g2} - V_{s2})}{r_{ds2} + r_s}$$

$$= \frac{V_o + g_m r_{ds2} (-V_{s2})}{r_{ds2} + r_s}$$

$$= \frac{V_o - g_m r_{ds2} i_o r_s}{r_{ds2} + r_s}$$

$$i_o (r_{ds2} + r_s + g_m r_{ds2} r_s) = \frac{V_o}{r_{ds2} + r_s}$$

$$\frac{V_o}{i_o} = \frac{r_{ds2} + r_s + g_m r_{ds2} r_s}{1}$$

output resistance is increased because, in order to make the mosfet to behave like ideal current source.

in series
one above other.


Date / /

saathi


$V_{min} \neq V_{DS2(min)} + I_D R_S$
but the swing

but the swing decreased.

Cascode current mirror

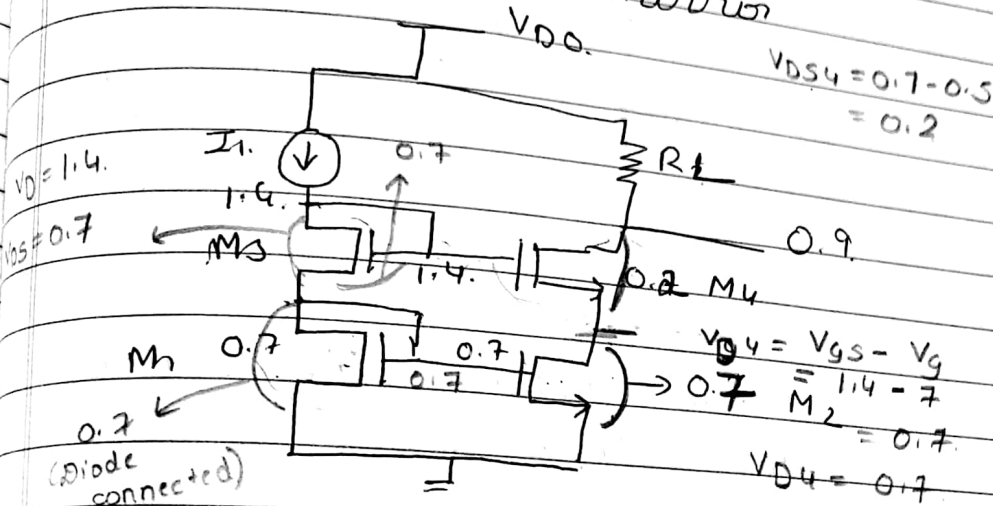

model

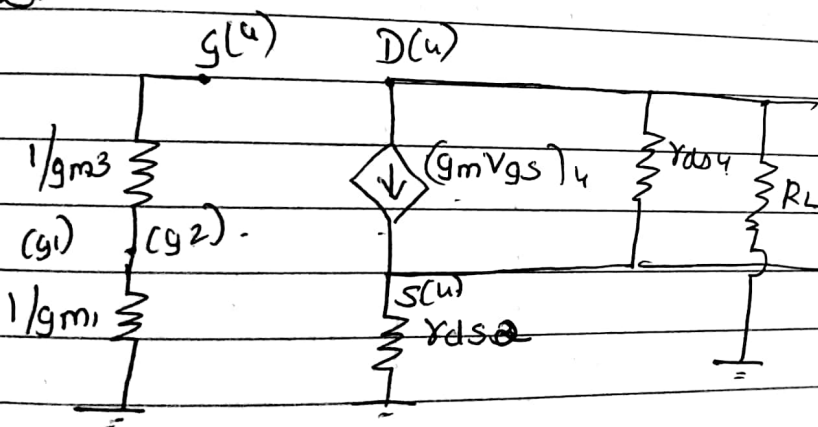

Applying KVL

$$V_0 - i_o r_{ds4} + (g_m v_{gs})_4 r_{ds4} - i_o r_{ds2} = 0$$

$$V_0 + (g_m V_{gs}) r_{ds4} = 10$$

$$V_O = i_o (r_{ds4} + r_{ds2}) \cdot g_m V_{gs4} r_{ds4}$$

$$V_o = i_o(r_{ds4} + r_{ds2}) + g_m(i_o r_{ds2}) r_{ds4}$$


$V_0 = 0$

$$\Rightarrow r_{ds4} = r_{ds2}$$

$$\Rightarrow 2r_{ds} + g_m r_{ds}^2$$

$$\Rightarrow r_{ds}(2 + g_m r_{ds}) = r_{ds}(2 + \mu)$$



Date ___/___/___

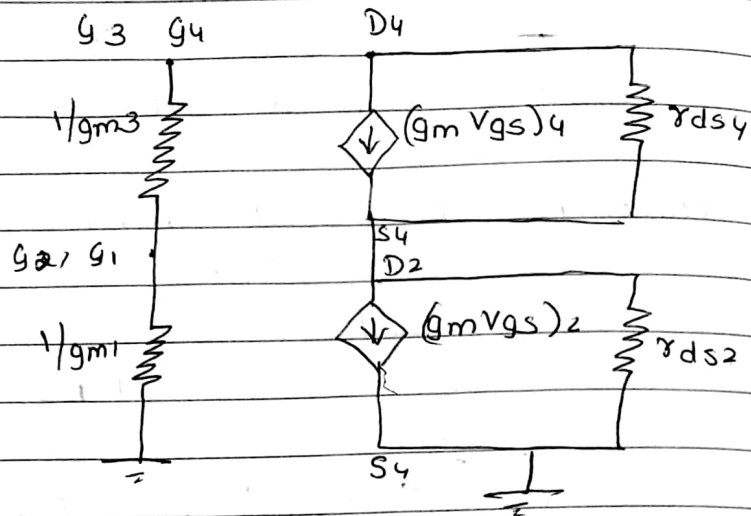

$$V_{GS2} = 0$$

M_2 is acting like source degenerating resistor.

→ Wilson current mirror:

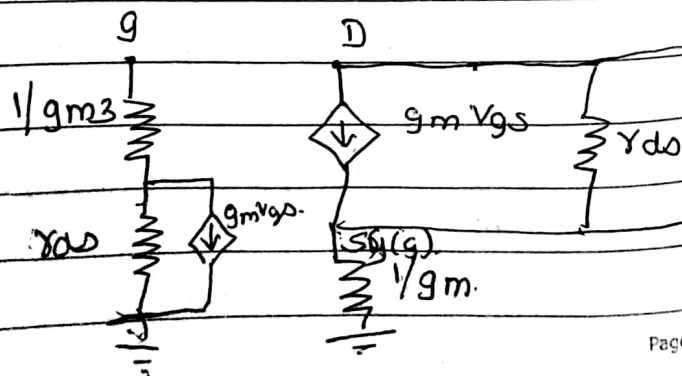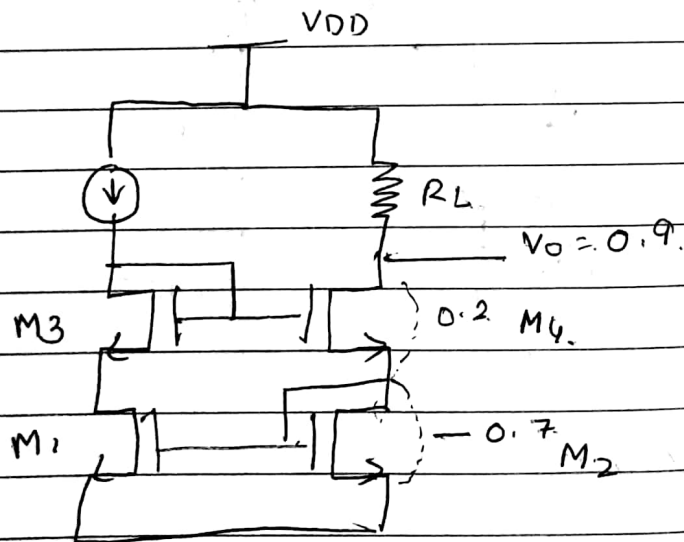

Page No. ___


Date ___/___/___

Saathi

$$R_0 = (2 + \mu) r_{ds}$$

$$V_0 = 0.9 - V_{DD}$$

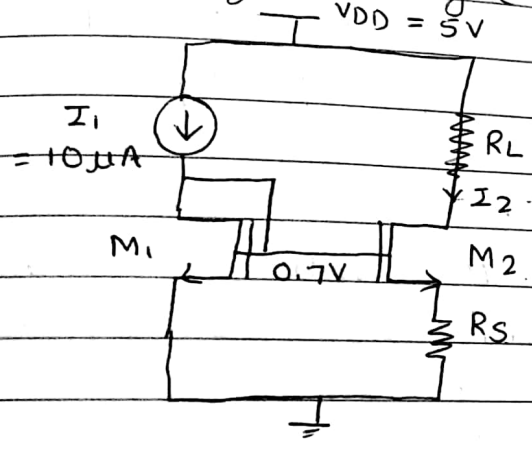1) For the widlar current mirror,
 $V_{DD} = 5V$, $V_{GS1} = 0.7V$, $V_{GS2} = 0.4V$,
 $I_1 = I_2 = 10\mu A$, $V_t = 0.2V$. Determine
the value of R_s , range of R_L &
output voltage swing ($V_{DSmin} = 0.2V$)



Draw a neat
ckt diagram
with labelled
values.

Q4. Given:- $V_{GS1} = 0.7V$ $V_{DD} = 5V$
 $V_{DS1} = 0.7V$
 $V_{GS2} = 0.4V$
 $(V_{DSmin})_2 = 0.2V$

$$V_{GS1} = V_{GS2} + I_2 R_s$$

$$R_s = \frac{0.7 - 0.4}{10 \times 10^{-6}}$$

$$= 0.3 \times 10^5$$

$$= 30 k\Omega$$

$$I_2 R_s = 10 \times 10^{-6} \times 30 \times 10^3 = 0.3$$

$$(V_0)_{min} = 0.2 + 0.3 = 0.5$$

Page No.

Date ____ / ____ / ____

Saathi

$$V_{DD} - I_2 R_L = V_O$$

$$V_{DD} - (V_O)_{\min} = I_2 R_L$$

$$(R_L)_{\min} = \frac{5 - 0.5}{10 \times 10^{-6}}$$

$$= 4.5 \times 10^5$$


$$= 450 \text{ k}\Omega$$

$$(V_O)_{\max} = V_{DD} = 5 \text{ V.}$$

$$\therefore (R_L)_{\min} = 0 \Omega$$

Range of R_L 0Ω to $450 \text{ k}\Omega$
for range of o/p voltage $0.5 - 5 \text{ V}$

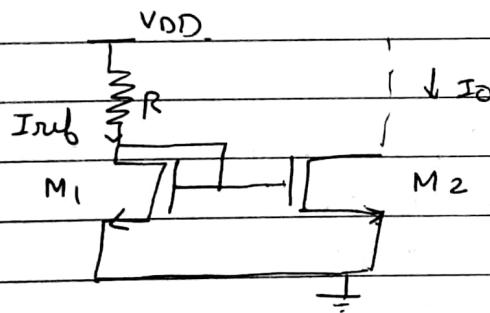2> Design the follⁿ C.M shown in below fig. $I_O = 100 \mu\text{A}$, $V_{DD} = 3 \text{ V}$
($\lambda = 0$), $V_t = 1 \text{ V}$, $k'_n (W/L) = 90 \text{ mA/V}^2$



sol. Given $I_O = 100 \mu\text{A}$ $V_{DD} = 3 \text{ V}$
 $V_t = 1 \text{ V}$

$$I_O = \frac{1}{2} k'_n \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$\frac{100 \times 10^{-6} \times 2}{90 \times 10^{-3}} = (V_{GS} - V_t)^2$$

$$2.22 \times 10^{-3} = (V_{GS} - V_t)^2$$

Page No.

Date / /

Saathi

$$(V_{GS})_1 - V_t = 0.047$$

$$(V_{GS})_2 = 1.047 \text{ V}$$

$$\therefore I_0 = I_{ref} = 100 \mu\text{A}$$

$$(V_{DS})_1 = 1.047 \text{ V}$$

$$\therefore \frac{V_{DD} - (V_{DS})_1}{I_{ref}} = R$$


$$\frac{3 - 1.047}{100 \times 10^{-6}} = R$$

$$R = 19.53 \text{ k}\Omega$$

3) For ckt shown below $V_{DD} = 5\text{V}$, $V_t = 1\text{V}$,
 $k'_n (= 20 \mu\text{A/V}^2)$, $R = 1 \text{ k}\Omega$

a) What is $(w/l)_1$ needed to obtain
 $I_{ref} = 1 \text{ mA}$

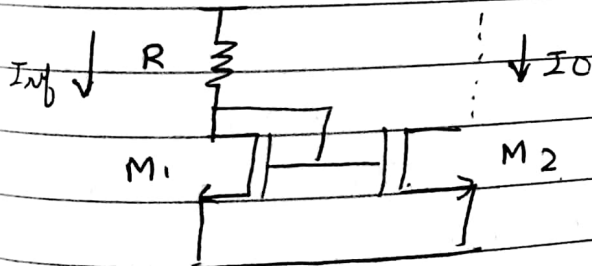b) What is $(w/l)_2$ for $I_0 = 7 \text{ mA}$
 $V_{DD} = 5\text{V}$



a) Given $I_{ref} = 1 \text{ mA}$

$$V_{DD} - I_{ref} R = (V_{DS})_1$$

$$(V_{DS})_1 = 5 - (1 \times 10^{-3})(1 \times 10^3)$$

$$= 4 \text{ V}$$

$$(V_{DS})_1 = (V_{GS})_1 = 4 \text{ V}$$

Date ____ / ____ / ____

Saathi

$$I_{ref} = \frac{1}{2} k'_n \left(\frac{W}{L}\right)_1 (V_{GS1} - V_t)^2$$

$$\frac{10 \times 10^{-3} \times 2}{20 \times 10^{-6} \times (4 - 1)^2}$$

$$\frac{100}{9} = \left(\frac{W}{L}\right)_1$$

b) $(V_{GS})_1 = (V_{GS})_2 = 4V$

$$I_0 = \frac{1}{2} k'_n \left(\frac{W}{L}\right)_2 (V_{GS2} - V_t)^2$$

$$\frac{7 \times 10^{-3} \times 2}{20 \times 10^{-6} \times (4 - 1)^2} = \left(\frac{W}{L}\right)_2$$

$$\frac{700}{9} = \left(\frac{W}{L}\right)_2$$


4) In width C.M $V_{GS1} = 0.7V$,
 $V_{GS2} = 0.4V$, $(V_{DS})_{2min} = 0.2V$, $V_{DD} = 5V$
 $I_1 = 10\mu A$, $R_L = 200k\Omega$. Determine
the value of I_2 for $(V_o)_{max} = 4V$.

a) also determine the value of R_S

b) If $(k'_n)_1 = (k'_n)_2 = 80\mu A/V^2$. Then
to get $I_2 = I_1 = 10\mu A$ what should
be aspect ratio of M_2 , if $(W/L)_1$
 $= 1$ ($V_t = 0.2V$).

Date / /

Saathi

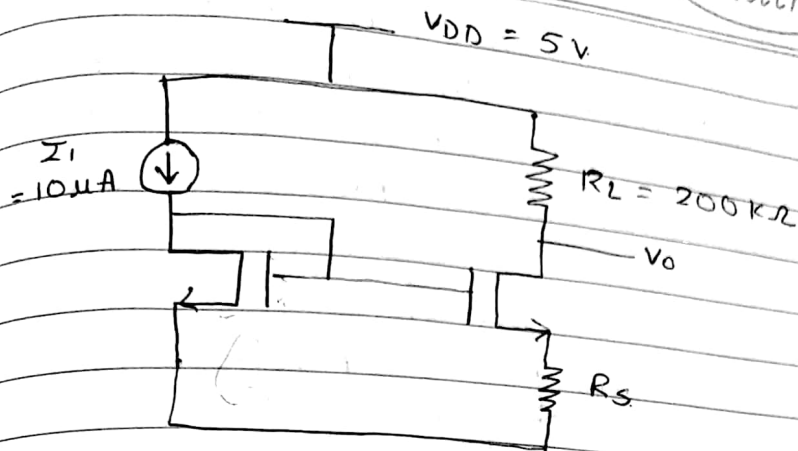

- a) Given $(V_{GS1}) = (V_{DS1}) = 0.7V$
 $(V_{GS})_2 = 0.4V$
 $(V_{DS})_{2 \min} = 0.2V$

$$I_O R_L = V_{DD} - (V_O)_{\max}$$

$$I_O = \frac{5 - 4}{200 \times 10^3}$$

$$I_O = 5 \mu A$$

$$V_{GS1} = V_{GS2} + I_O R_S$$

$$(10/5) \times 10^{-6} \quad 0.7 - 0.4 = R_S$$

$$\frac{0.3 \times 10^6}{5} = R_S$$

$$60 k\Omega = R_S$$


$$I_2 = I_1$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_t)^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_t)^2$$

$$\left(\frac{W}{L} \right)_2 = \frac{(0.7 - 0.2)^2}{(0.4 - 0.2)^2} = \frac{25}{4} = 6.25$$


- 5) In a basic current mirror determine the mirror ratio when $V_{GS} = 2V$, $(V_{DS})_2 = 10V$, $\lambda = 0.02/V$. Assume both mosfet's are identical.

Sol:

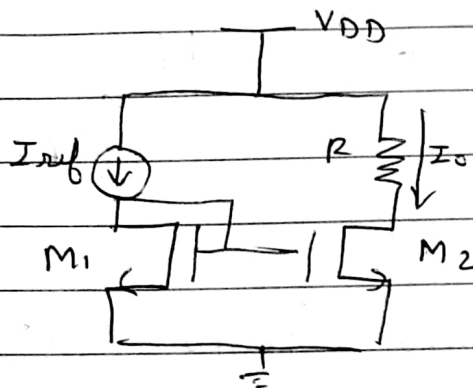

$$\begin{aligned} \frac{I_O}{I_{ref}} &= \frac{(\mu/L)_2 (1 + \lambda V_{DS2})}{(\mu/L)_1 (1 + \lambda V_{DS1})} \quad \left| \begin{array}{l} (V_{GS})_1 = \\ (V_{DS})_1 = 2V \end{array} \right. \\ &= \frac{1 + (0.02)(10)}{1 + (0.02)(2)} \\ &= \frac{1 + 0.2}{1 + 0.04} \\ &= 1.15 \end{aligned}$$

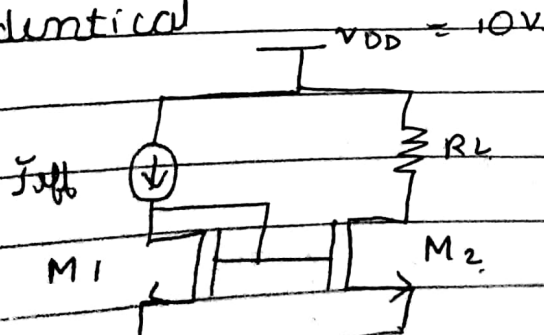- 6) Calculate the o/p current I_2 for the basic current mirror, if $V_{DD} = 10V$, $\mu_n C_{ox} (\mu/L) (1 + \lambda V_{DS}) = 250 \mu A/V^2$, $V_t = 1V$, $\lambda = 0.0133/V$. $I_{ref} = 150 \mu A$, $V_{DS2} = 10V$. Assume mosfet's are identical.



Date ___/___/___

Saathi

$$\mu_n C_{ox} \left(\frac{W}{L} \right) (1 + \lambda V_{DS})$$

$$I_{ref} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (1 + \lambda V_{DS}) (V_{GS1} - V_t)^2$$

$$\frac{150 \times 10^{-6} \times 2}{250 \times 10^{-6}} = (V_{GS1} - V_t)^2$$

$$1.2 = (V_{GS1} - V_t)^2$$

$$1.095 = V_{GS1} - V_t$$


$$V_{GS1} = 2.095 \text{ V}$$

$$V_{GS1} = V_{GS2} = 2.095$$

$$\begin{aligned} \frac{I_O}{I_{ref}} &= \frac{\frac{1}{2} \times \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}}{1 + (0.0133)(2.095)} \\ &= \frac{1 + (0.0133)(2.095)}{1 + (0.0133)(2.095)} \end{aligned}$$

$$I_O = 165.34 \mu\text{A}$$

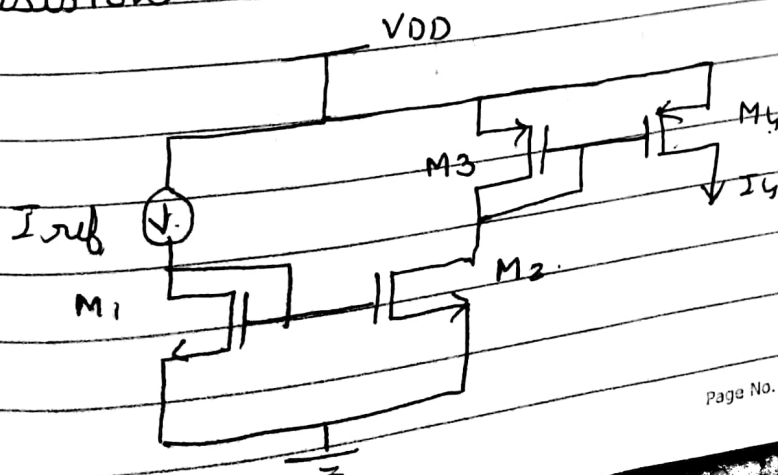Find the drain current of M_4 in the given circuit, where all transistors are in saturation region.



Page No.

Date ___ / ___ / ___

Sol:-
$$\frac{I_2}{I_{ref}} = \frac{(\omega/l)_2 \cdot (1 + \lambda V_{DS2})}{(\omega/l)_1 \cdot (1 + \lambda V_{DS1})}$$

assume $\lambda = 0$

$$I_2 = I_{ref} \left(\frac{(\omega/l)_2}{(\omega/l)_1} \right) \quad \text{--- (1)}$$

WKT $I_2 = I_3$


$$I_4 = \frac{(\omega/l)_4}{(\omega/l)_3} I_3$$

$$I_4 = \frac{(\omega/l)_4}{(\omega/l)_3} I_3$$

$$I_4 = \frac{(\omega/l)_4}{(\omega/l)_3} I_3$$


$$I_4 = \frac{(\omega/l)_4}{(\omega/l)_3} \times \frac{(\omega/l)_2}{(\omega/l)_1} \times I_{ref}$$

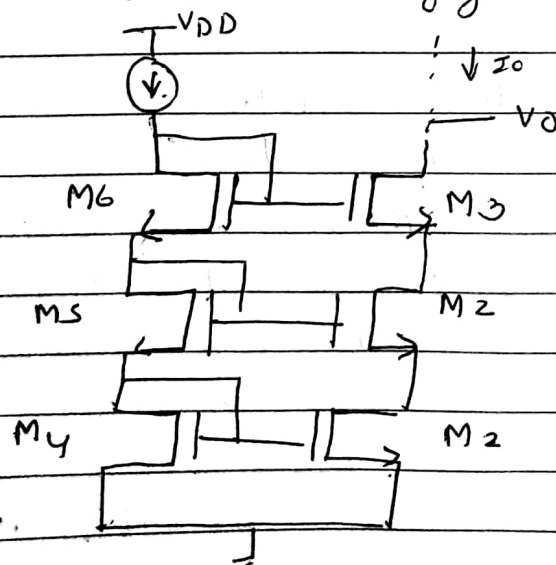Q8) Determine the o/p resistance of double cascode current mirror shown in below figure



Date ___/___/___

Saathi

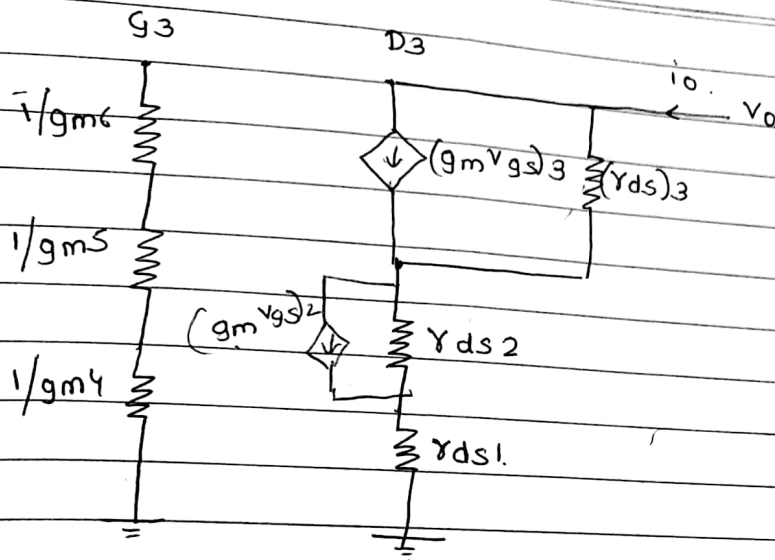

$$V_o - i_o(r_{ds})_3 + (g_m V_{gs})_3 r_{ds3} - i_o(r_{ds})_2 - i_o(r_{ds})_1 + (g_m V_{gs})_2 r_{ds2} = 0$$

$$V_o - i_o(r_{ds3} + r_{ds2} + r_{ds1}) + (g_m V_{gs})_3 r_{ds3} = 0$$

$$V_{gs3} = (V_g - V_s)_3$$

$$= V_g - ($$

$$V_{gs2} = V_g - V_s$$

$$= 0 - I_o r_{ds1}$$

$$V_{gs3} = V_g - [(g_m V_{gs})_2 r_{ds} + I_o r_{ds2} + I_o r_{ds1}]$$